

# Low Energy Design Techniques for Data Converters


Harijot Singh Bindra

Researcher, Integrated Circuit Design  
*University of Twente, Enschede, The Netherlands*

# Overview

- **Motivation**
  - Input Buffer Requirement
- **Reducing Input Drive Current**
- **Low power single supply buffered SAR ADC**
  - Proposed Solution
  - Integration of Buffer with SAR ADC
  - Offset Correction
- **Measurement Results**
- **Conclusion**

# Motivation

 


- Overall low energy ( $E_{IN} + E_{ADC}$ ) consumption

# Overview

- **Motivation**
  - **Input Buffer Requirement**
- **Reducing Input Drive Current**
- **Low power single supply buffered SAR ADC**
  - **Proposed Solution**
  - **Integration of Buffer with SAR ADC**
  - **Offset Correction**
- **Measurement Results**
- **Conclusion**

# Motivation – Input Buffer

 


Low Power ( $V^2/Z_{OUT}$ )

Low Noise ( $kT/C_S$ )  
(Large  $C_S$ )

$$Z_{OUT} > Z_{IN}$$

# Motivation – Input Buffer

 


$$Z_{\text{OUT}} \gg Z_{\text{IN}}$$


$$V_{\text{IN,ADC}} \approx 0$$

**Low power sensor cannot drive ADC input**

# Motivation – Input Buffer

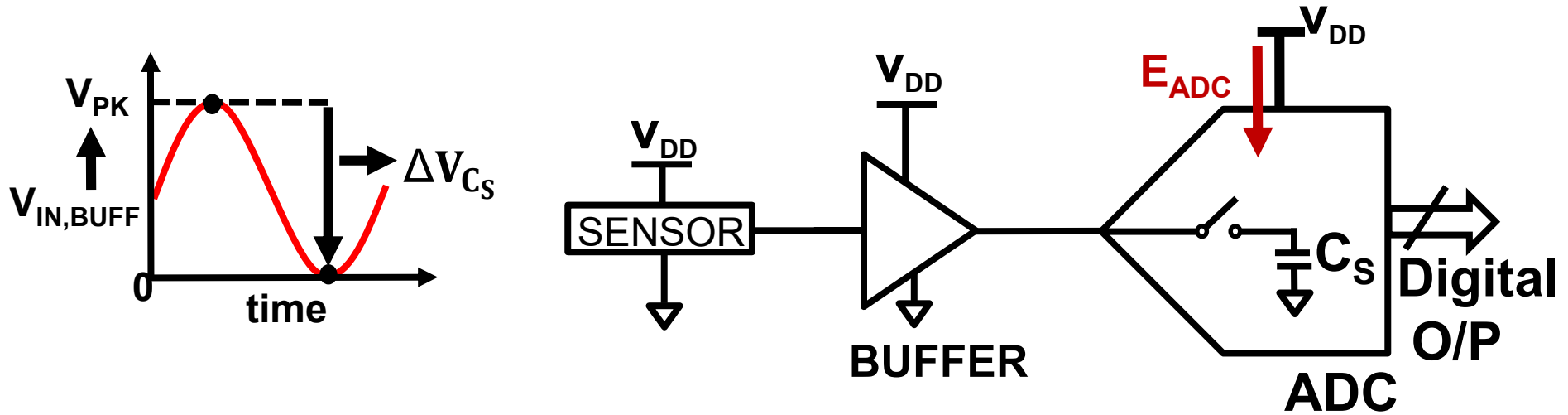

# Motivation – Input Buffer Requirement

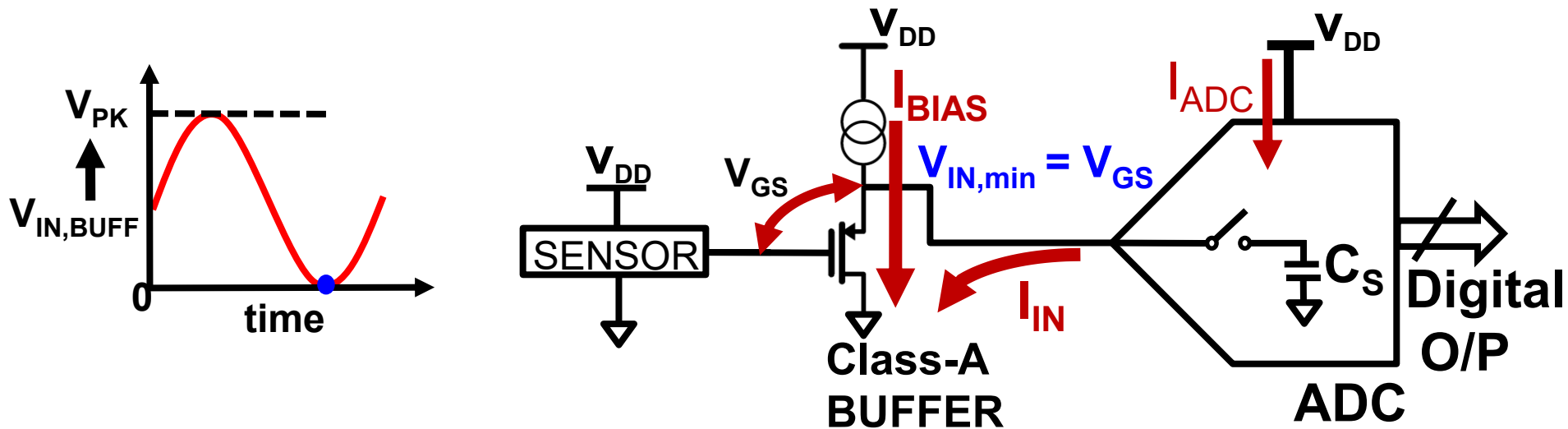


😊 Class-A buffer : low distortion, always “ON” output stage.

☹  $V_{IN,min} > V_{GS}$ . Rail-to-rail operation not feasible with single supply.




# Motivation – Input Buffer Requirement

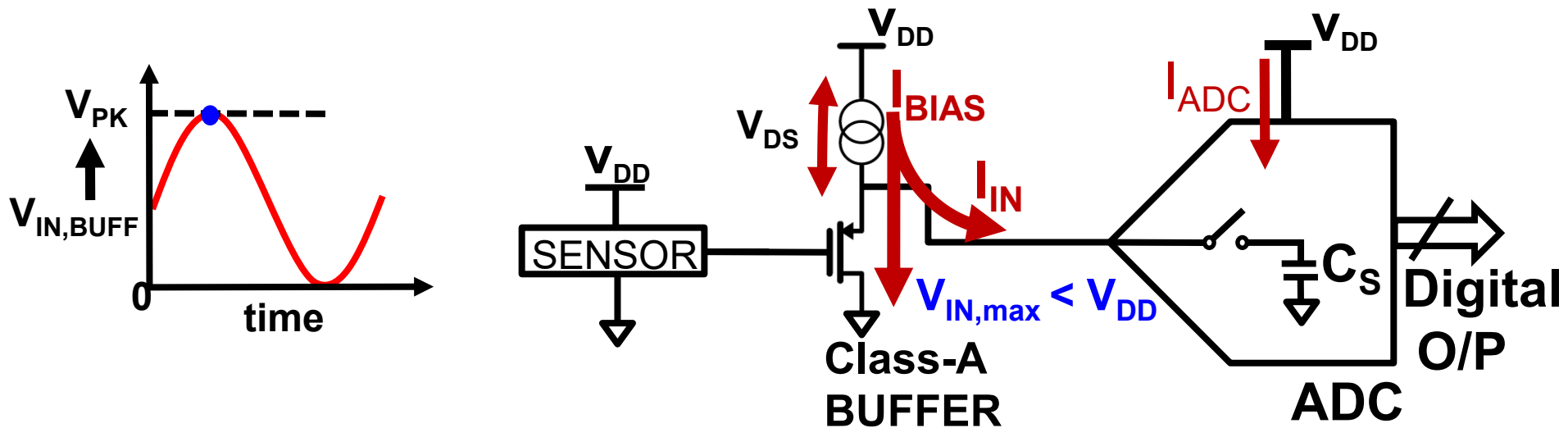

⊖  $I_{BIAS} \geq I_{IN,MAX}$  and  $V_{IN,max} < V_{DD} - V_{DS}$


⊖ Power hungry and poor efficiency.  $P_{BUFF} \geq V_{PK} I_{BIAS}$
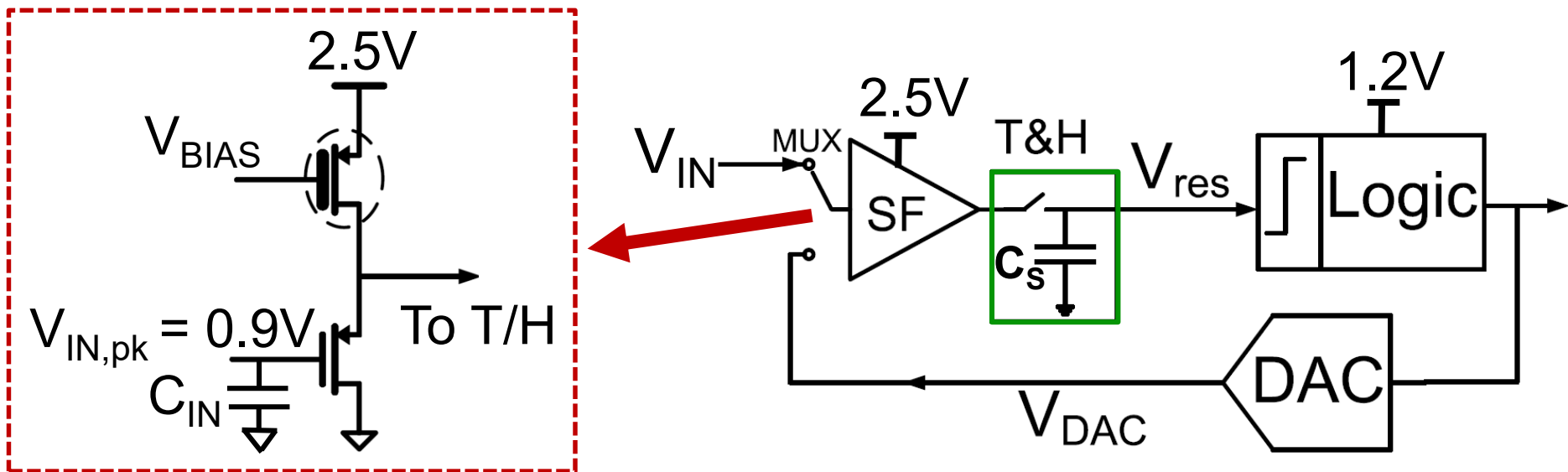
# Prior Art - Source Follower embedded in SAR




- 😊 Input capacitance ( $C_{IN}$ ) is 0.2pF (18x lower than  $C_s$ )
- 😞 Additional high supply voltages ( $\approx 3xV_{PK}$ ) required

# Motivation – Input Buffer Requirement

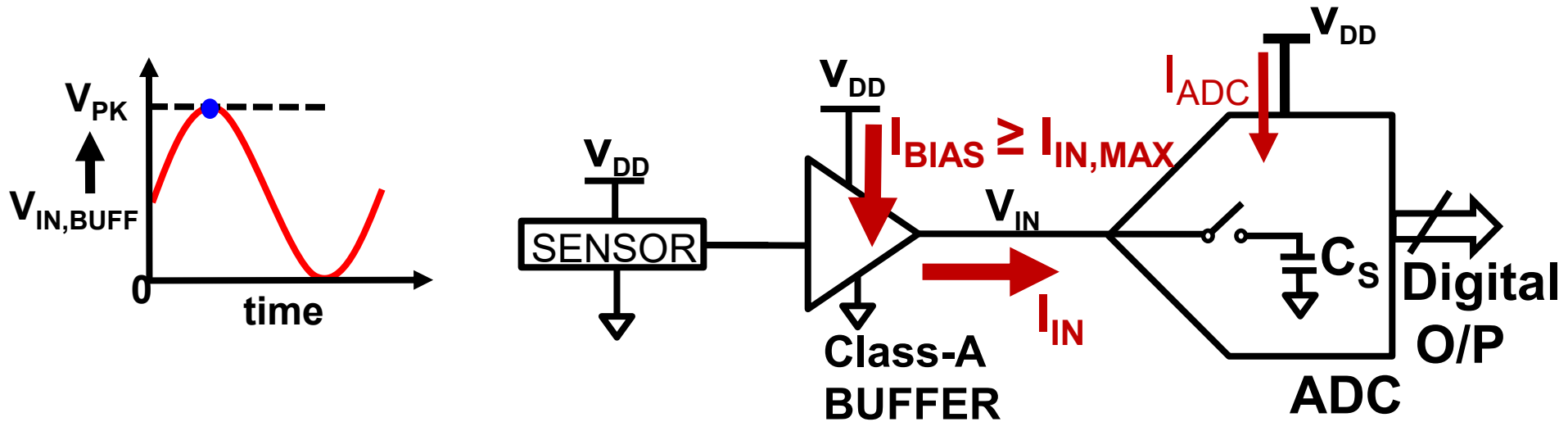

- Walden FoM (incl. buffer),  $FoM_{W,buff} = (P_{ADC} + P_{BUFF}) / (f_s \cdot 2^{ENOB})$
- $P_{BUFF} \uparrow \rightarrow FoM_{W,buff} \uparrow$

# Motivation – Input Buffer Requirement

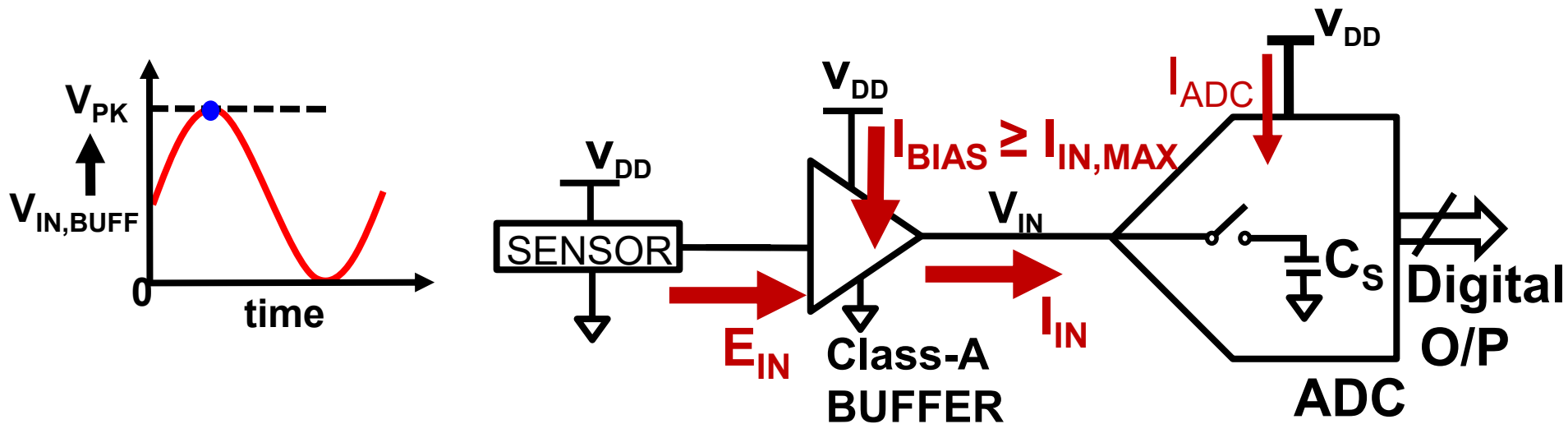


- Single  $V_{DD}$  with near rail-to-rail signal swing.
- Minimize  $I_{BIAS}$  (or  $I_{IN,MAX}$ )  $\rightarrow$  low  $FoM_{W,buff}$ .
- Minimize  $E_{IN}$ .

# Overview

- **Motivation**
  - Input Buffer Requirement
- **Reducing Input Drive Current (A-SSCC 2017)**
- **Low power single supply buffered SAR ADC**
  - Proposed Solution
  - Integration of Buffer with SAR ADC
  - Offset Correction
- **Measurement Results**
- **Conclusion**


# Conventional

- $V_{INP}$  sampled on  $C_{DAC+}$

 


- $V_{INN}$  sampled on  $C_{DAC-}$
- Peak Sampling current,  $I_{PK} = V_{PK}/R_{SH}$

# Conventional

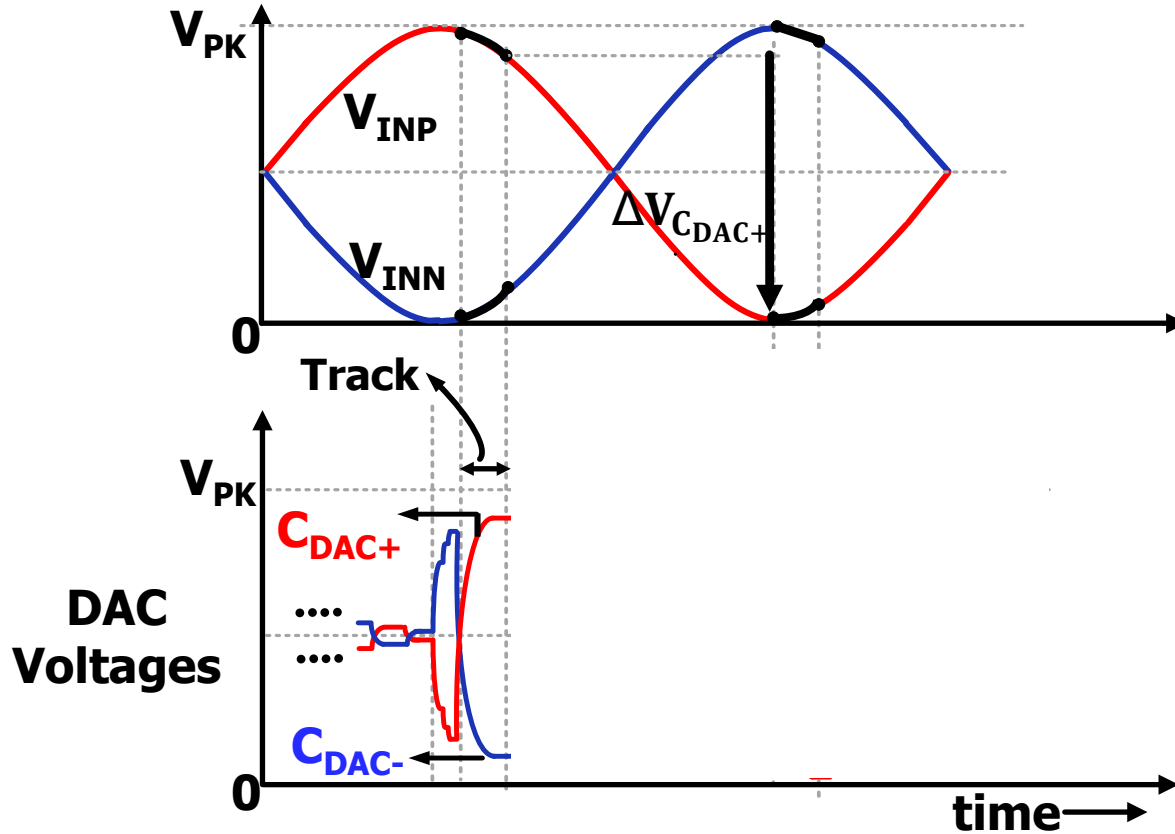


# Conventional

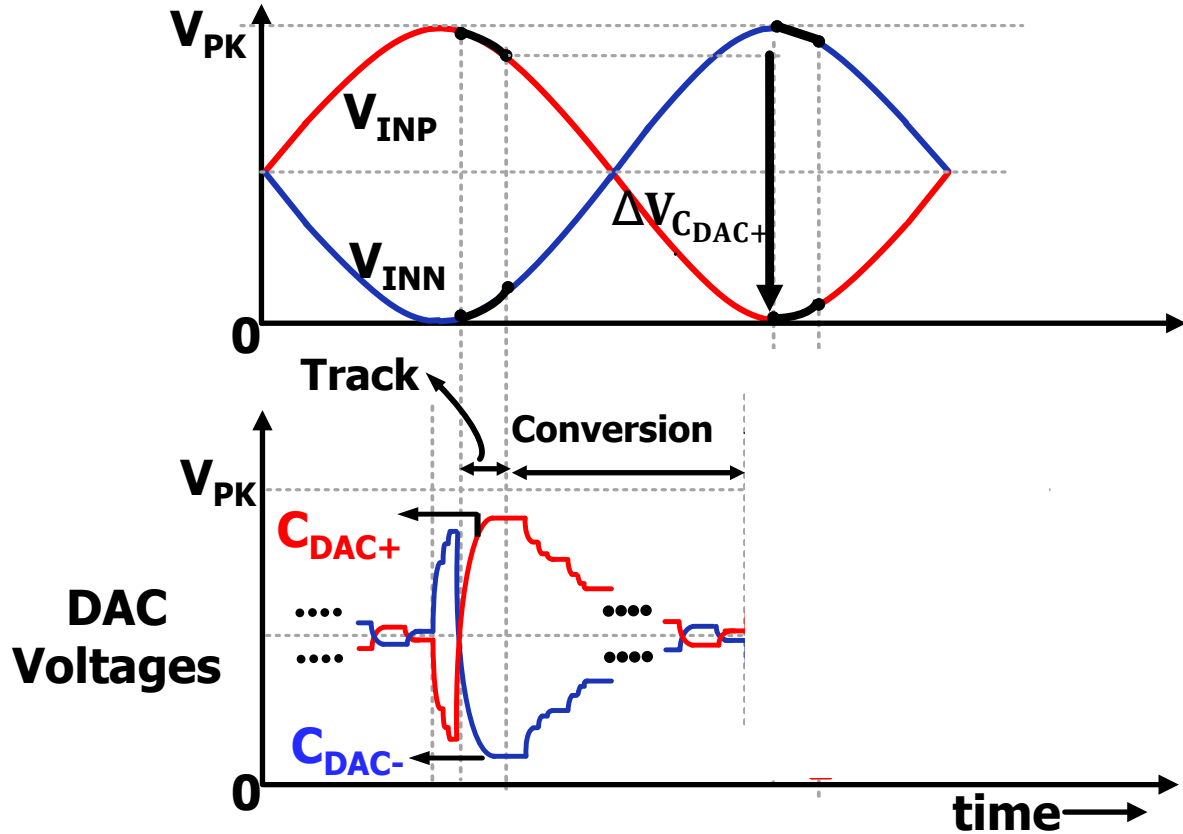




# Conventional

 
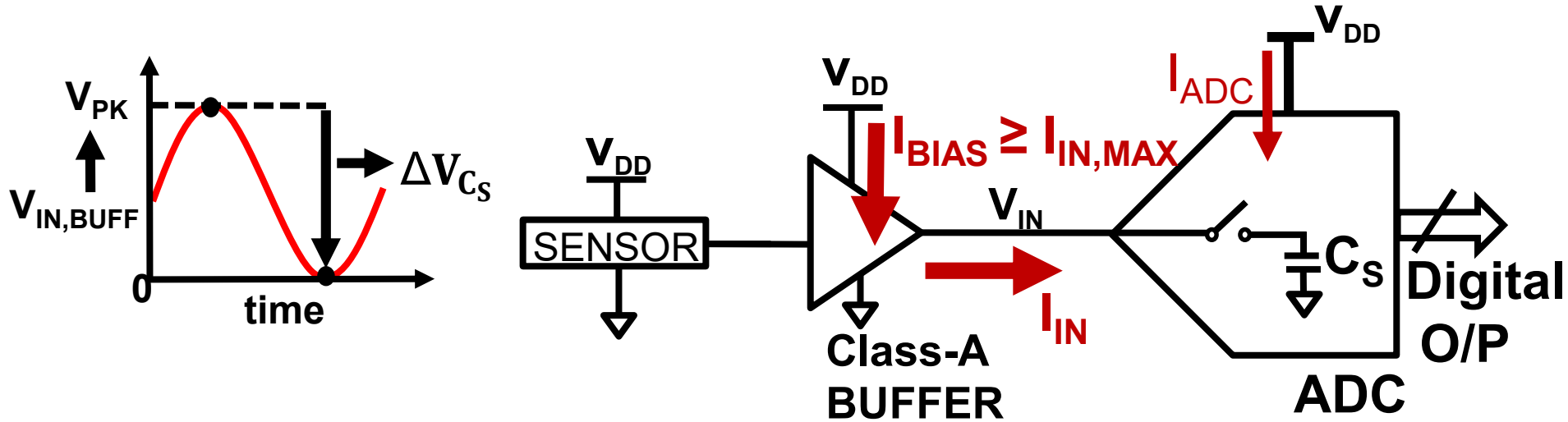
# Reducing $\Delta V_{C_S}$ and Input Current




□ For Nyquist rate ADCs,  $\Delta V_{C_S} \leq V_{PK}$

□  $I_{IN,MAX} = (N \cdot C_S \cdot V_{PK} / T_{TRACK})$

[ $N = 0.69(\#Bits)$ ]
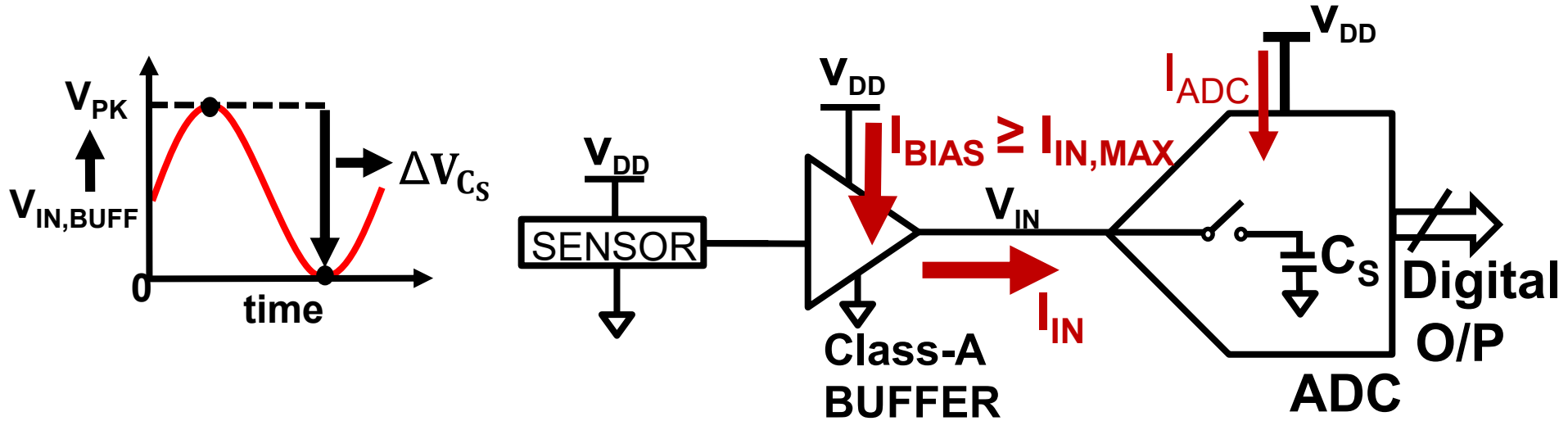
# Reducing $\Delta V_{C_S}$ and Input Current





- Linear Settling

- $I_{IN,MAX} = (N \cdot C_S \cdot \Delta V_{C_S} / T_{TRACK})$

- $I_{IN,MAX} \Downarrow \longrightarrow \Delta V_{C_S} \Downarrow$

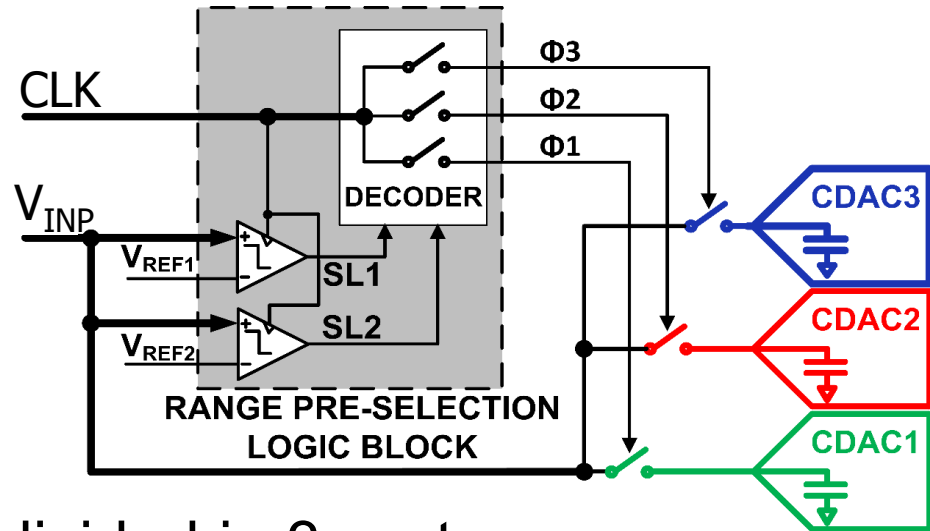
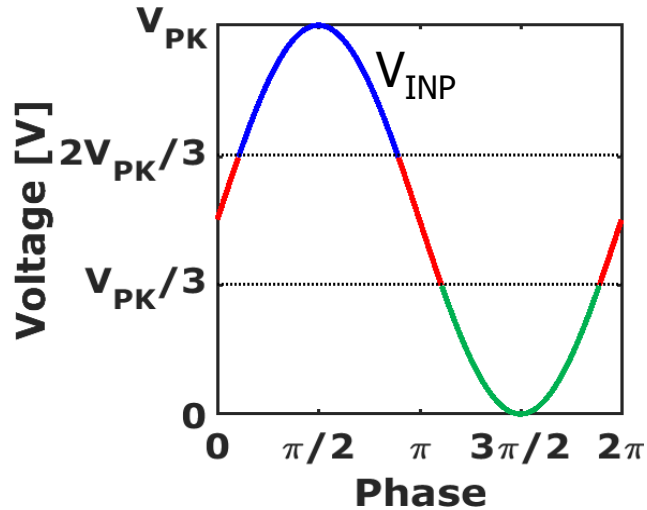
# Reducing $\Delta V_{C_S}$ and Input Current





- Full-scale range of  $V_{INP}$  divided in 3-parts
  - Each sub-range of  $V_{INP}$  sampled onto the respective CDAC
  - Limits the  $\Delta V_{C_S}$  to  $V_{PK}/3$

[ Bindra, ASSCC 2017 ]

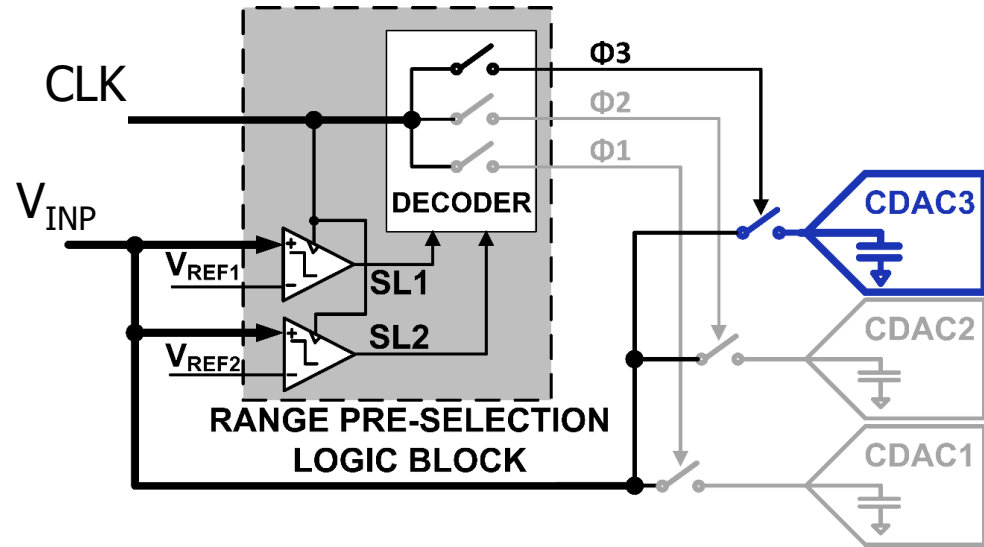
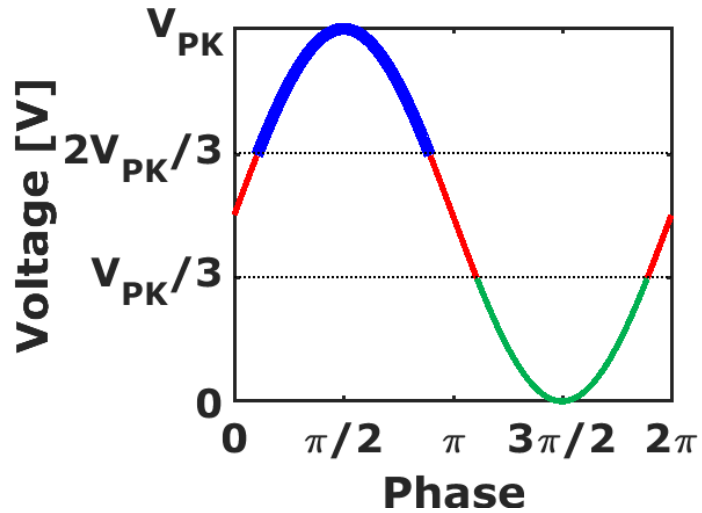
# Reducing $\Delta V_{C_s}$ and Input Current



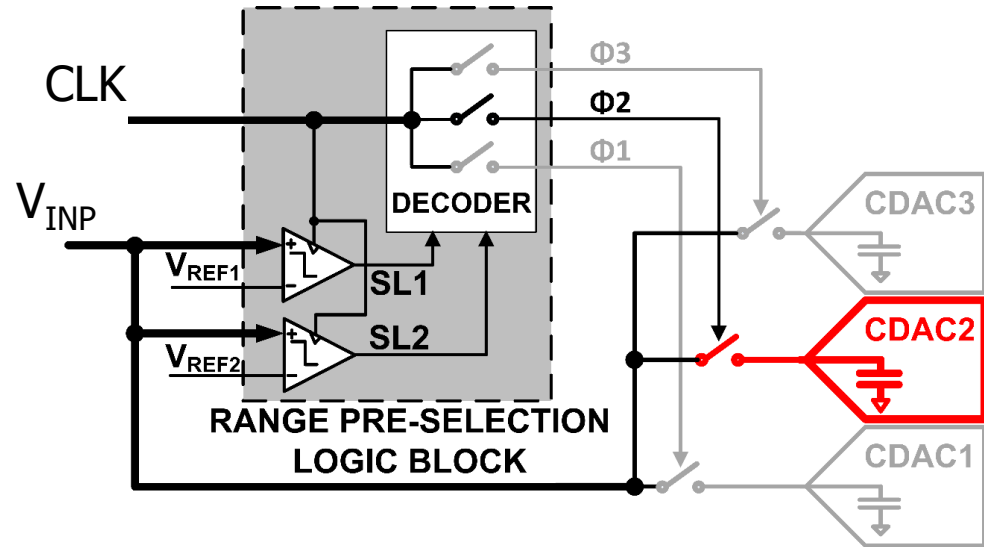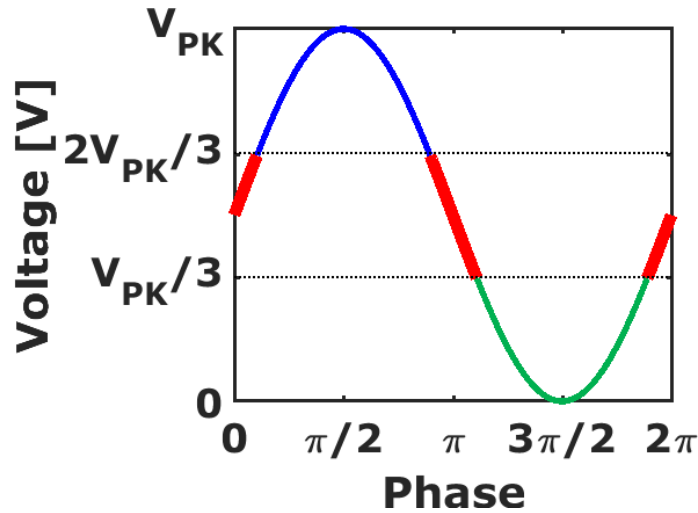
# Reducing $\Delta V_{C_s}$ and Input Current


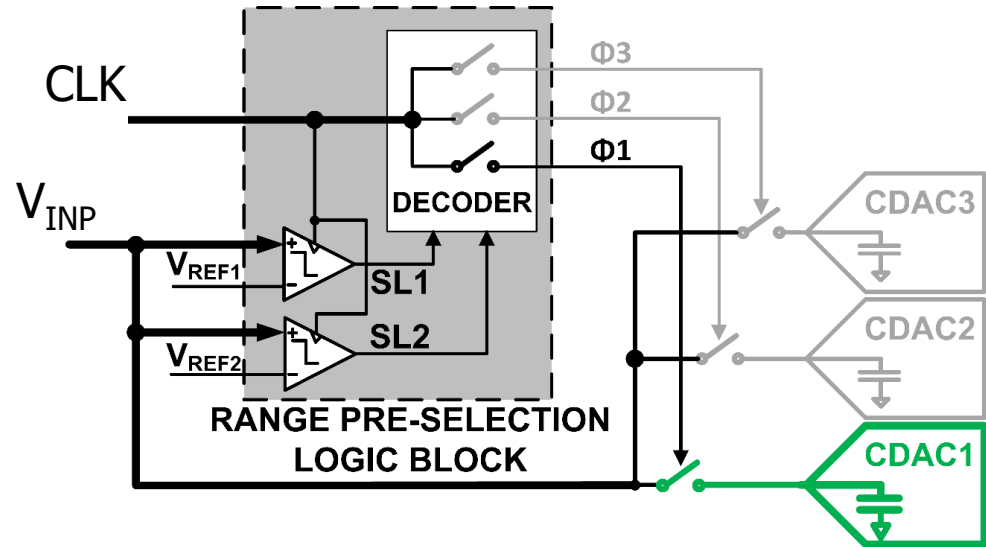 
# Reducing $\Delta V_{C_s}$ and Input Current




# Measurement - Input Sampling Current

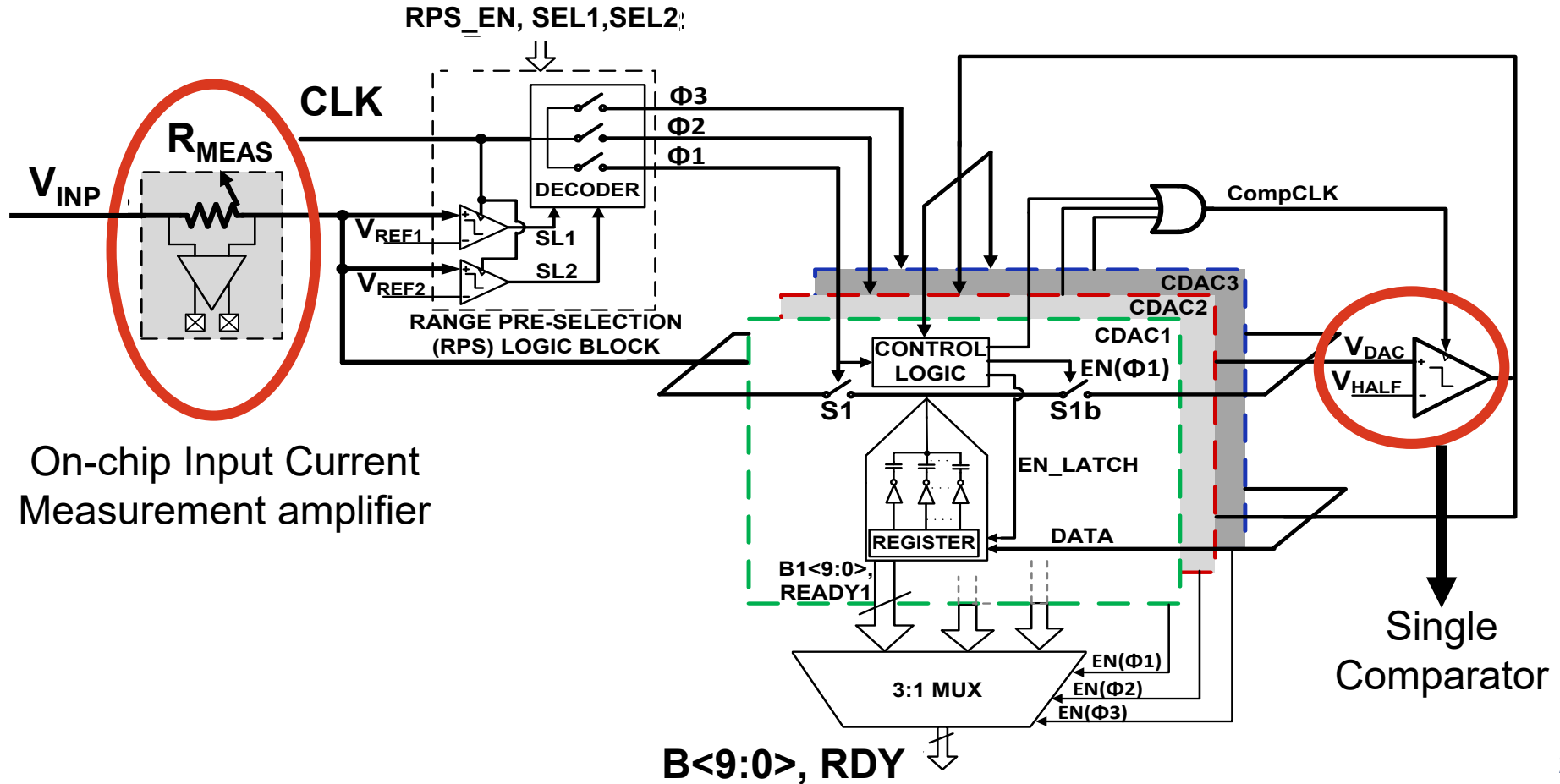




# Die micrograph (65nm CMOS)

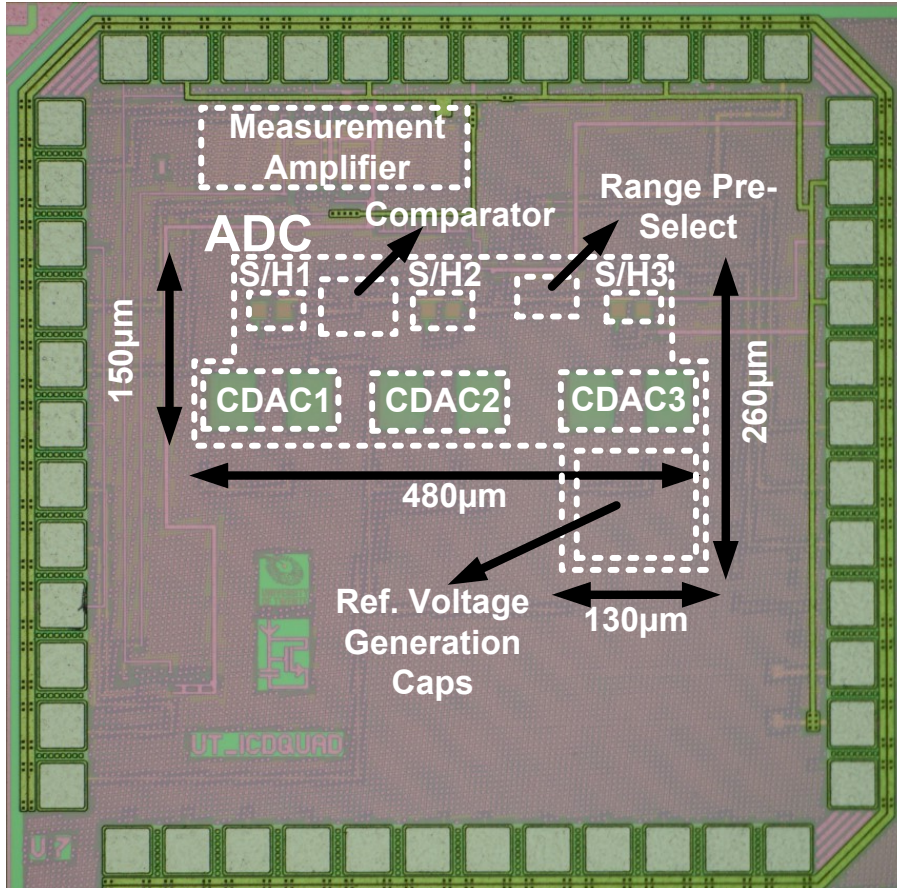


- Area –  $0.08\text{ mm}^2$  (including decaps)
- Measurement amplifier to compare input sampling current
- CDACs not selected act as decap (connected to single reference voltage)

# Measurements- Input Sampling Current

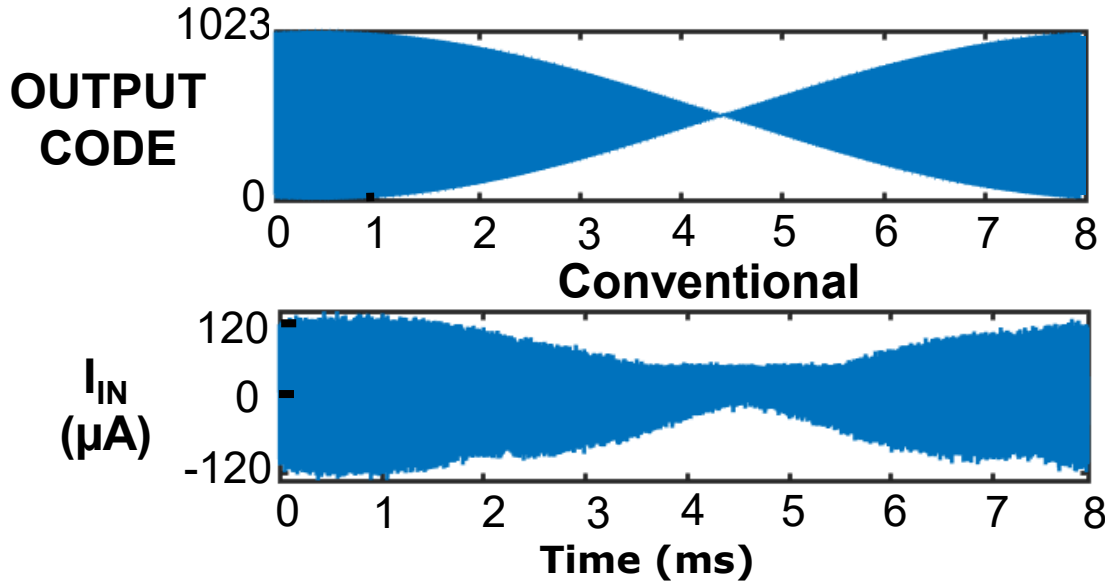


- $f_s = 2MS/s$  and  $f_{IN} = 999.9375kHz$
- Beat frequency =  $f_s/2 - f_{IN} = 62.5$  Hz
- $I_{IN} = \Delta V_{C_s} / (R_{MEAS} + R_{SH})$
- $R_{MEAS} + R_{SH} \leq 1 / [(N+1) \cdot C \cdot 10 \cdot f_s]$

# Measurements- Input Sampling Current

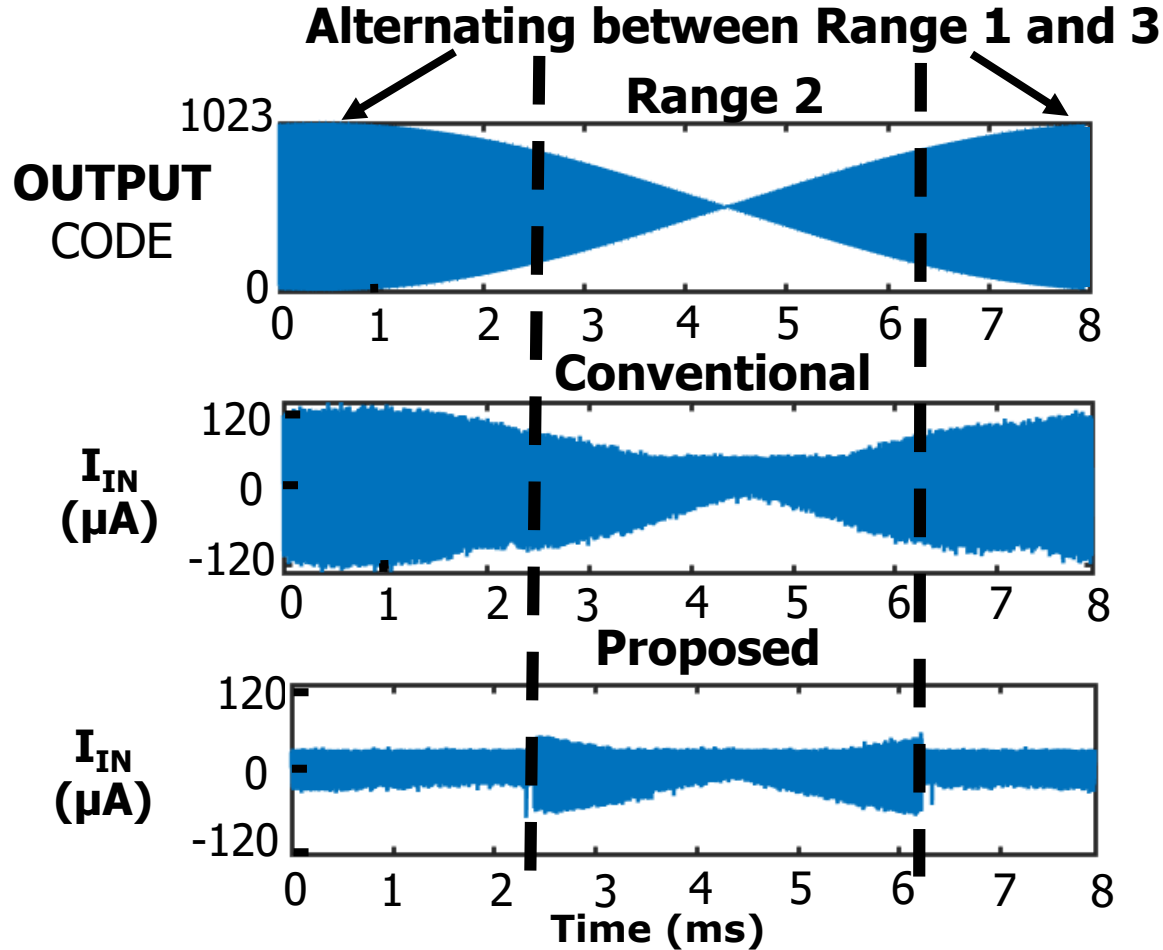
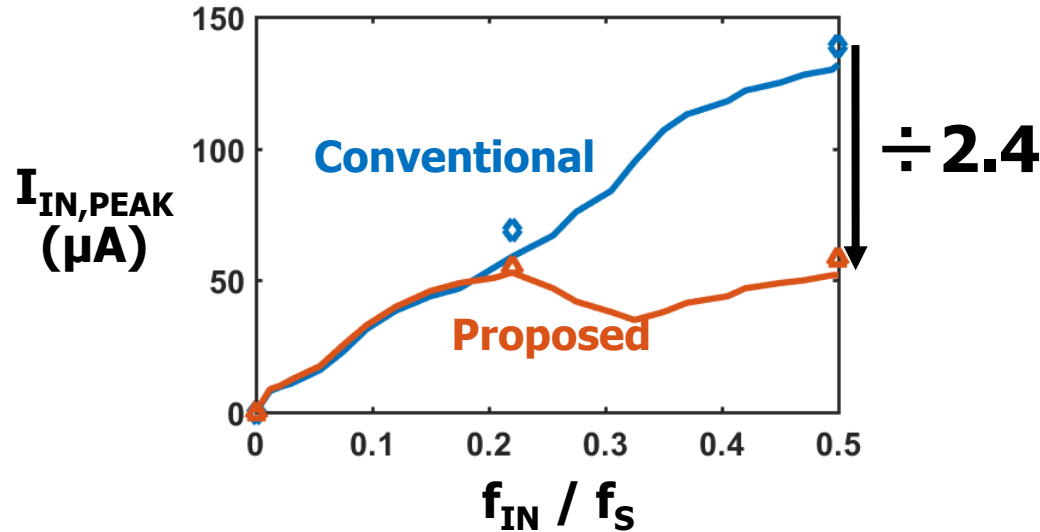
# Reducing $\Delta V_{C_S}$ and Input Current




😊 Reduced  $\Delta V_{C_S}$  reduces peak input sampling current.


# Overview

- Motivation
  - Input Buffer Requirement
- Reducing Input Drive Current
- **Low power single supply buffered SAR ADC (CICC 2019)**
  - Proposed Solution
  - Integration of Buffer with SAR ADC
  - Offset Correction
- Measurement Results
- Conclusion



# Conventional Architecture

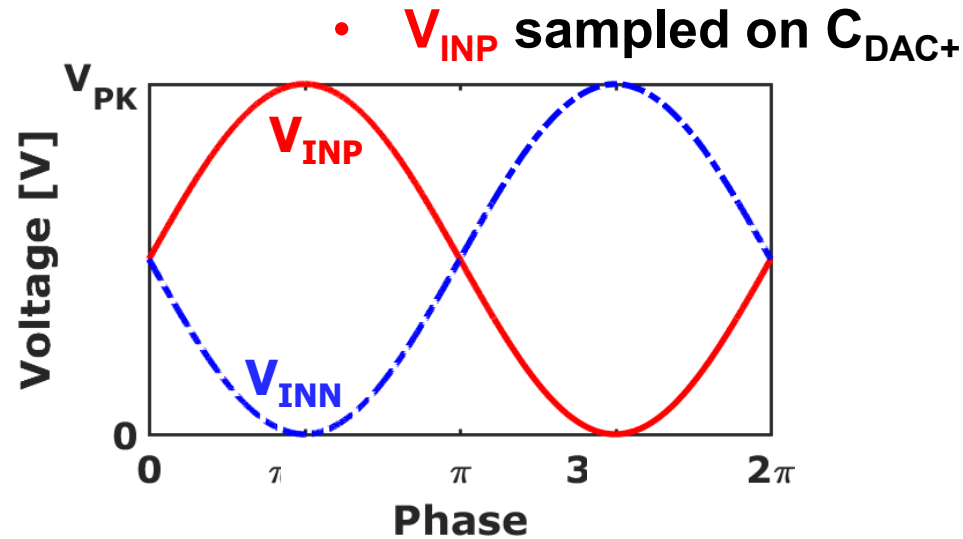

- $V_{INN}$  sampled on  $C_{DAC-}$

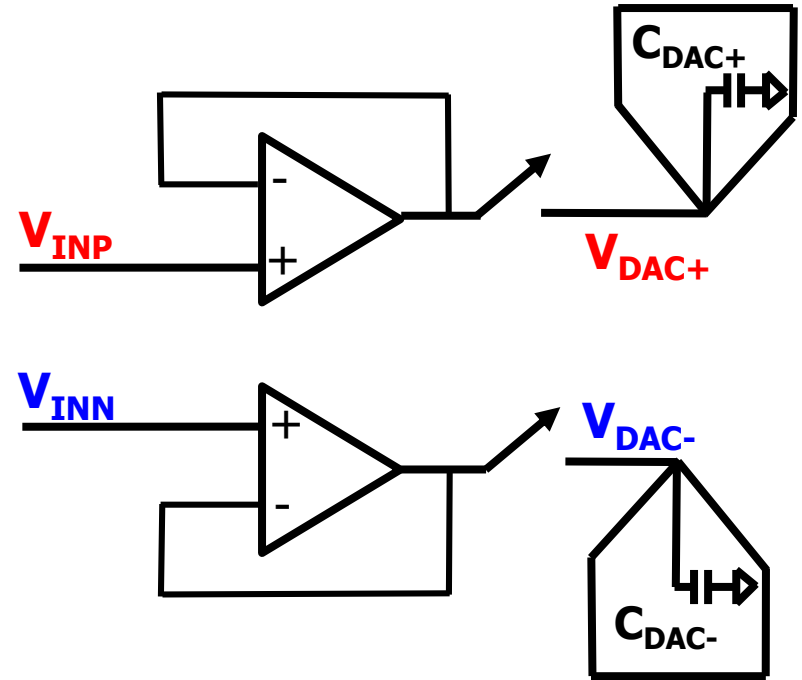

# Conventional Architecture

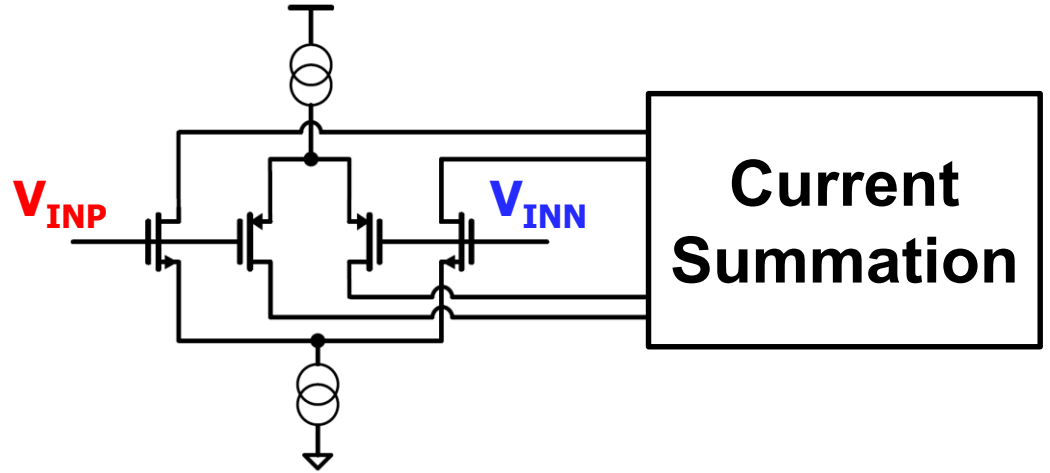 

- 😊 Complimentary input pair can handle rail-to-rail input.
- ☹️ Distortion due to signal dependent gm variation and offset modulation.


[ Huijsing, JSSC 1980 ]

# Overview

- Motivation
  - Input Buffer Requirement
- Reducing Input Drive Current
- **Low power single supply buffered SAR ADC (CICC 2019)**
  - **Proposed Solution**
  - Integration of Buffer with SAR ADC
  - Offset Correction
- Measurement Results
- Conclusion




# Architecture - Front End

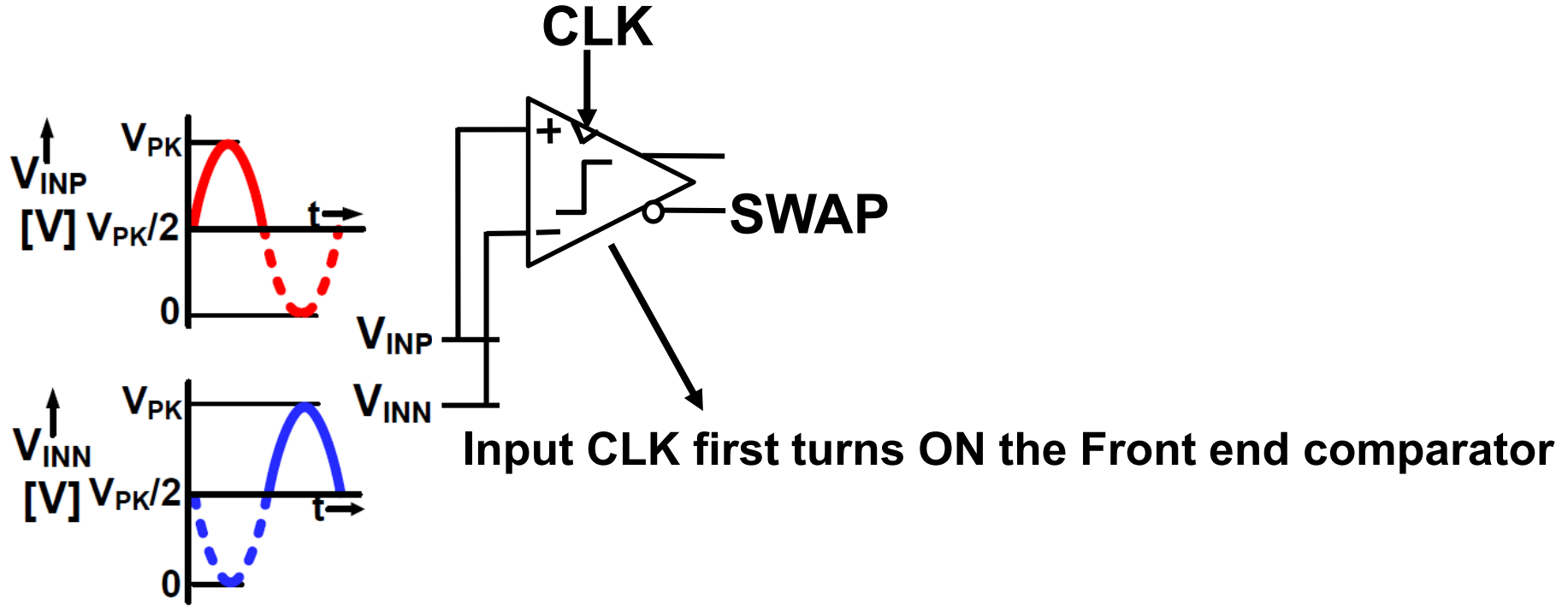


[ Bindra, *CICC 2019* ]


# Architecture - Front End

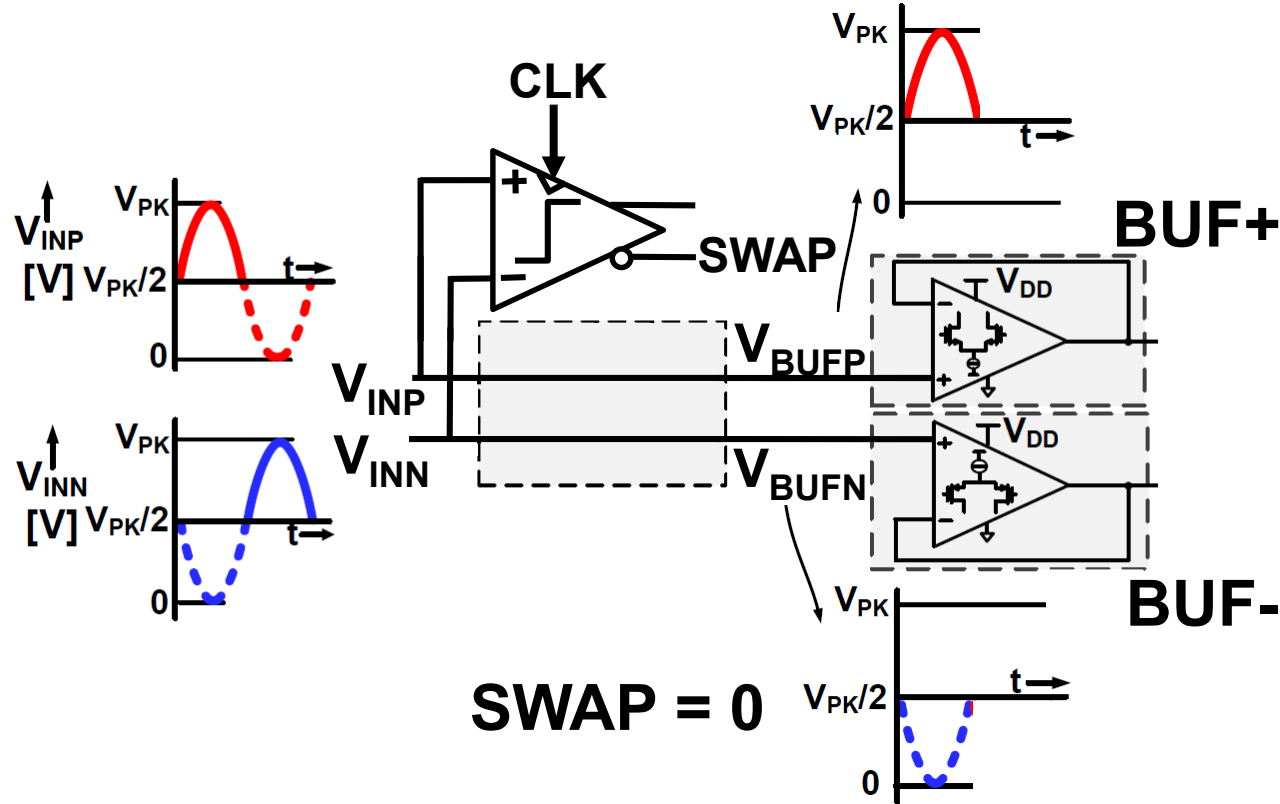


# Architecture - Front End

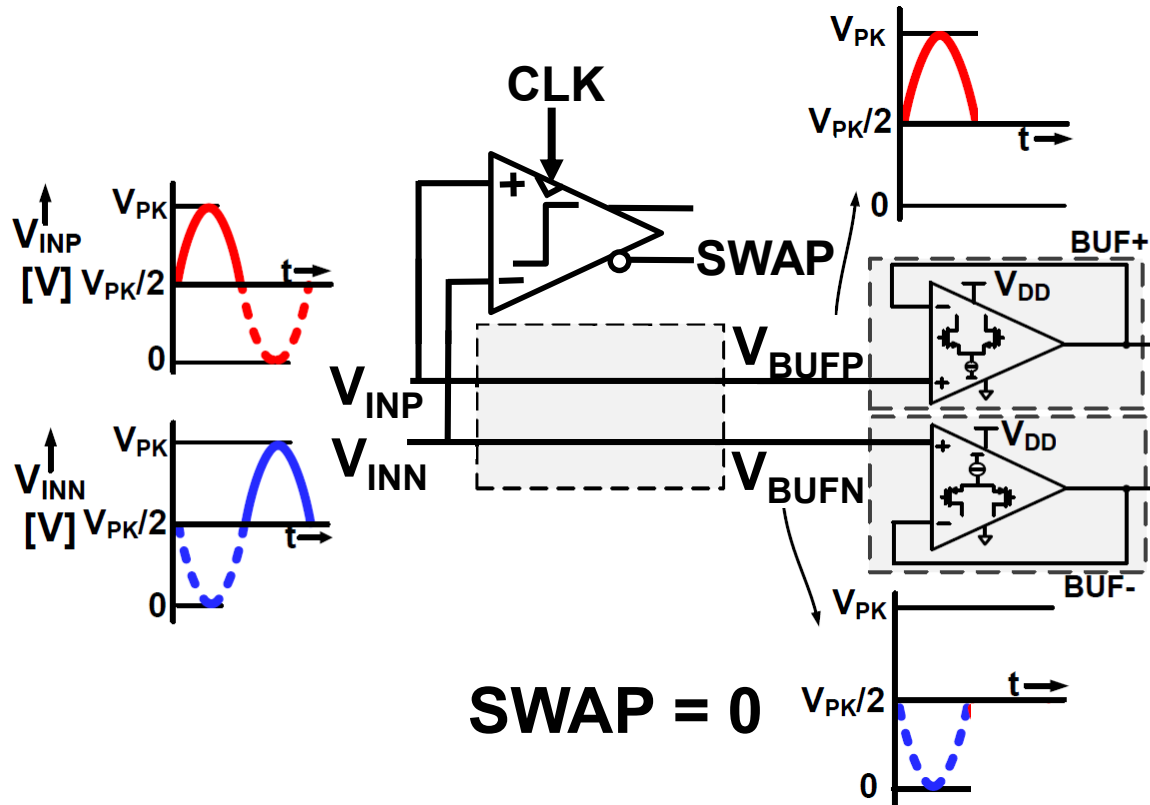


**BUF+**

 


**$V_{DD} \approx V_{PK}$  BUF-**

 


# Architecture - Front End

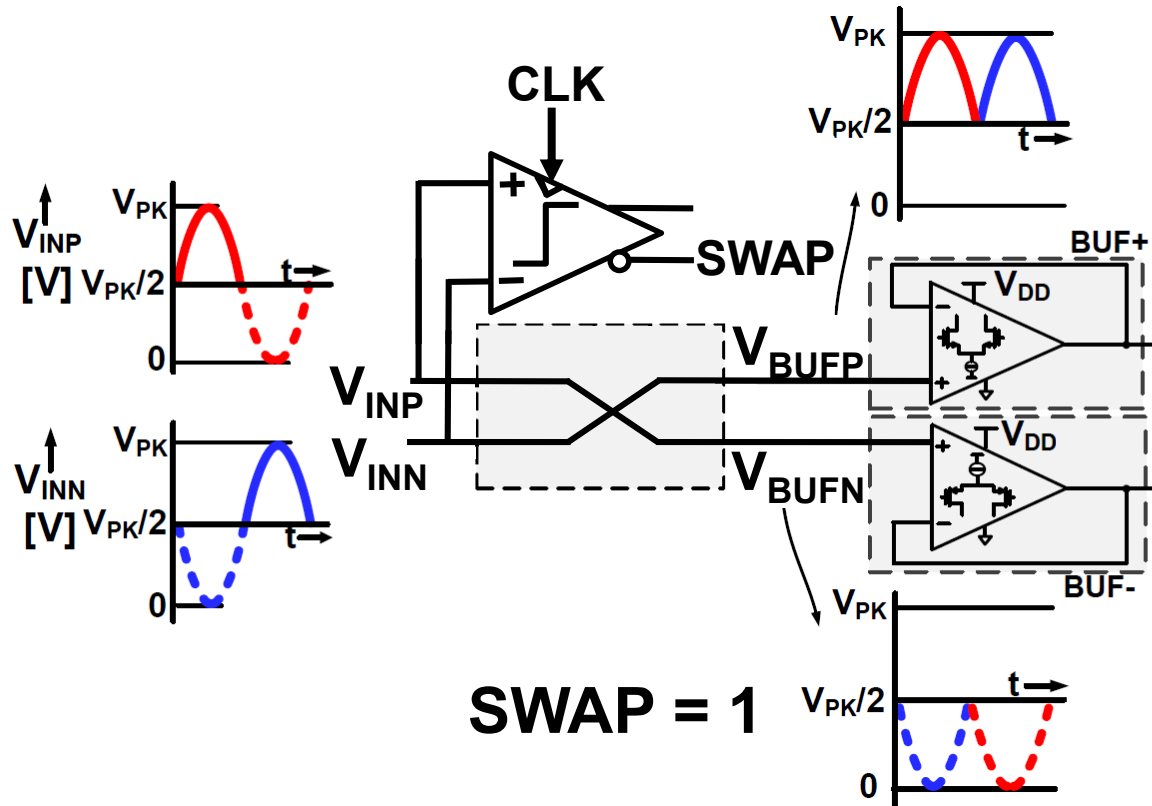


**BUF+**

 

**$V_{DD} \approx V_{PK}$  BUF-**

 


# Architecture - Front End

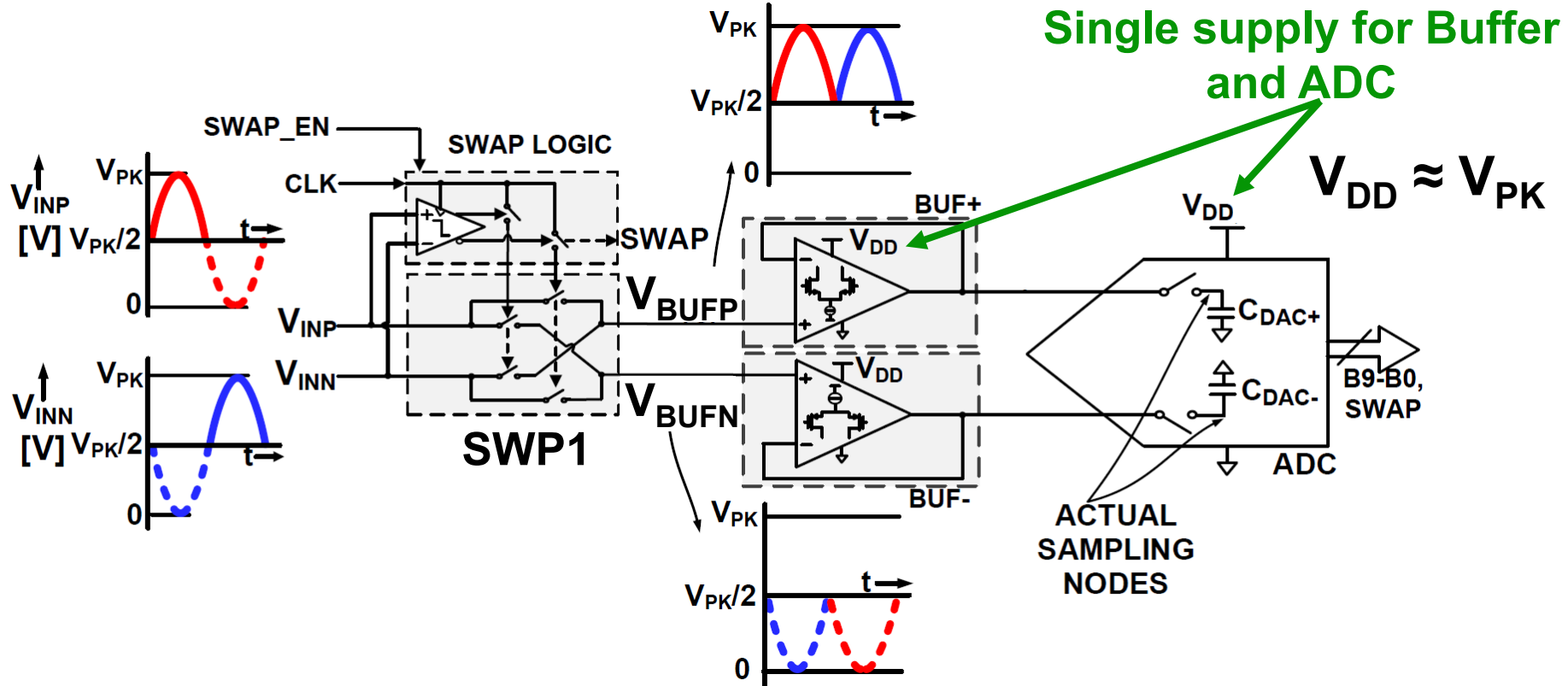

# Overview


- Motivation
  - Input Buffer Requirement
- Reducing Input Drive Current
- **Low power single supply buffered SAR ADC (CICC 2019)**
  - Proposed Solution
  - **Integration of Buffer with SAR ADC**
  - Offset Correction
- Measurement Results
- Conclusion
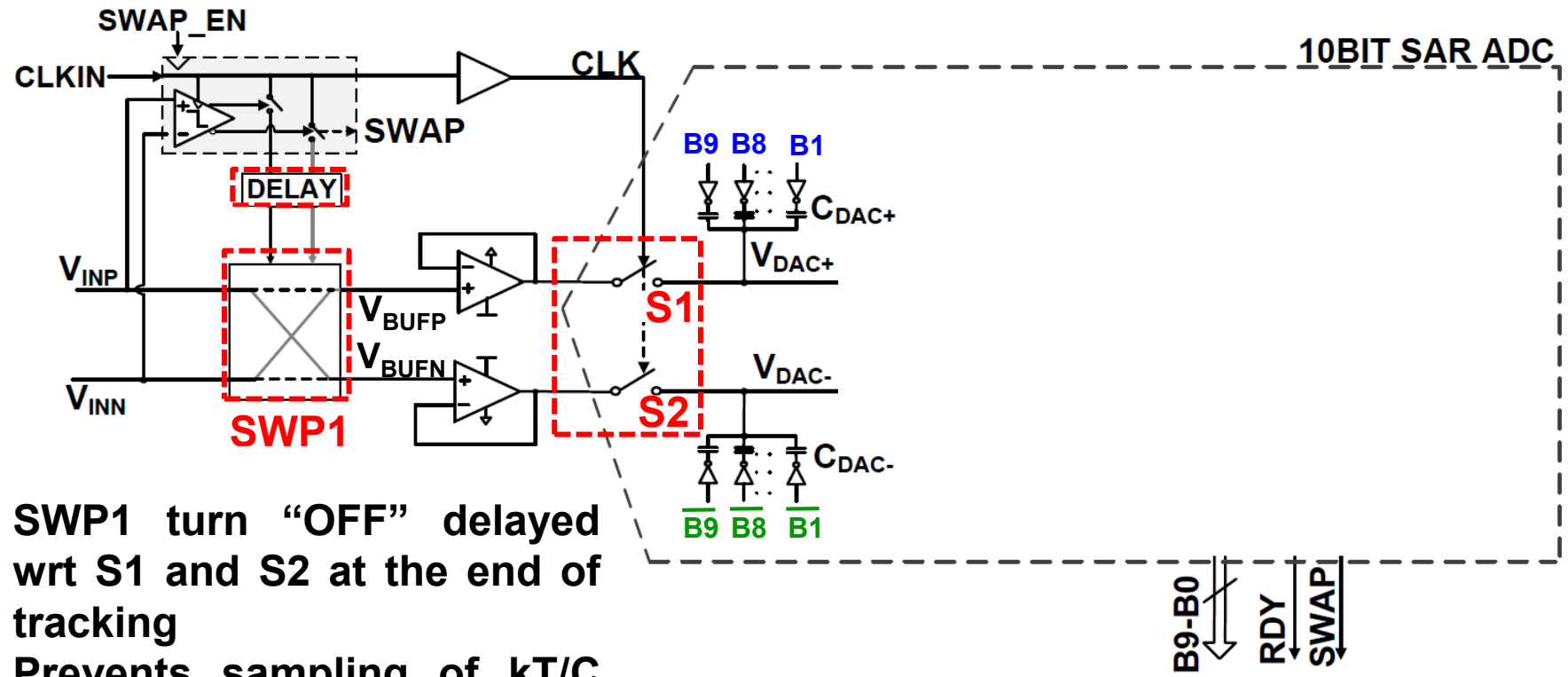
# Architecture - Buffers integrated with ADC




- **SWP1** turn "OFF" delayed wrt **S1** and **S2** at the end of tracking
- Prevents sampling of  $kT/C$  noise at the buffer's input
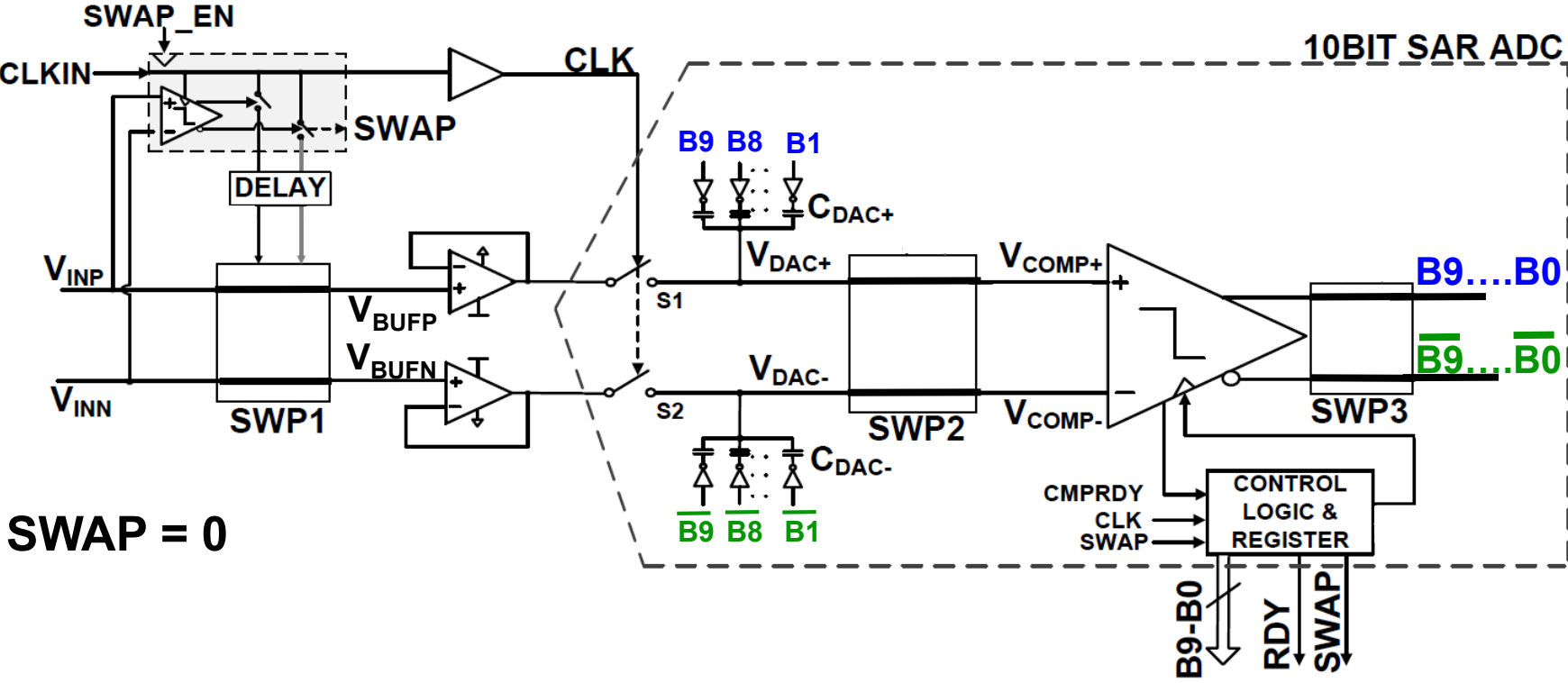
# Architecture - Buffers integrated with ADC





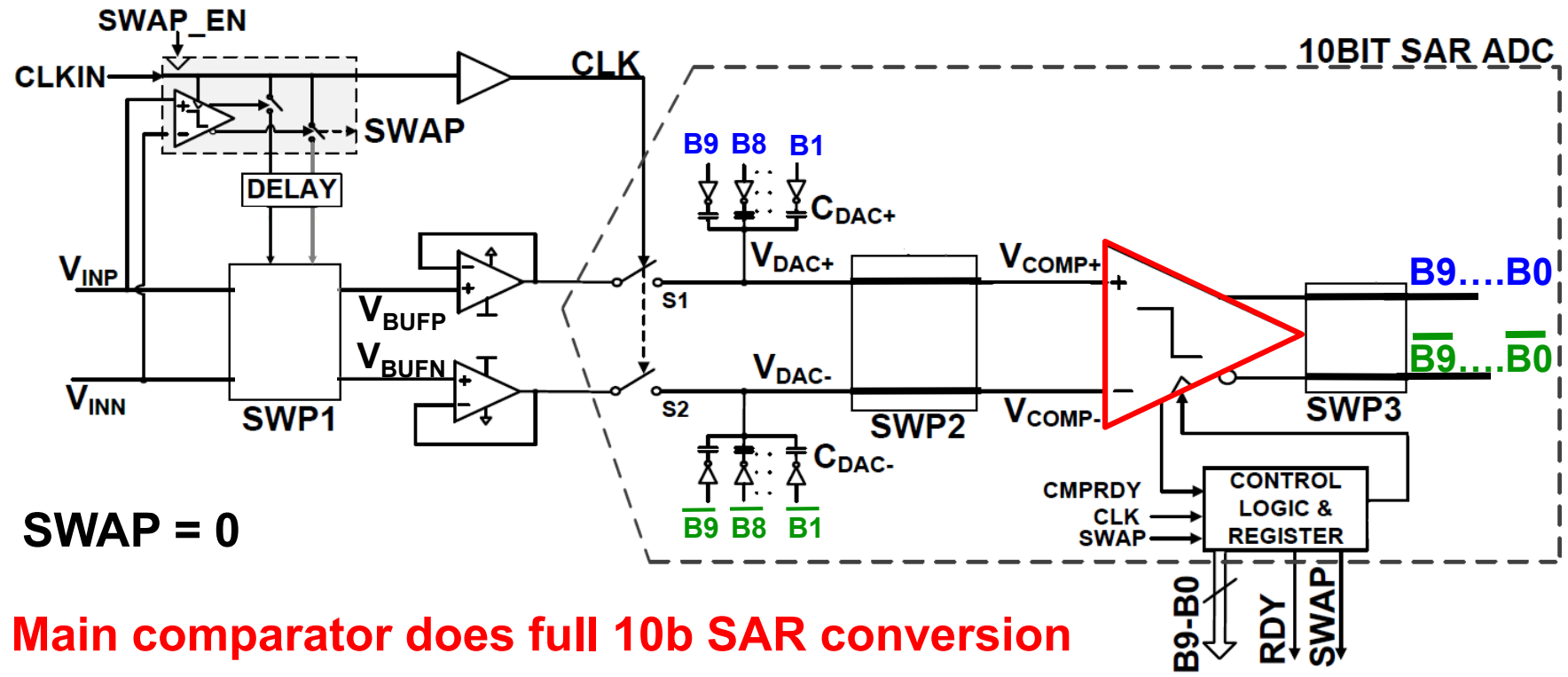
# Architecture - Buffers integrated with ADC




Main comparator does full 10b SAR conversion
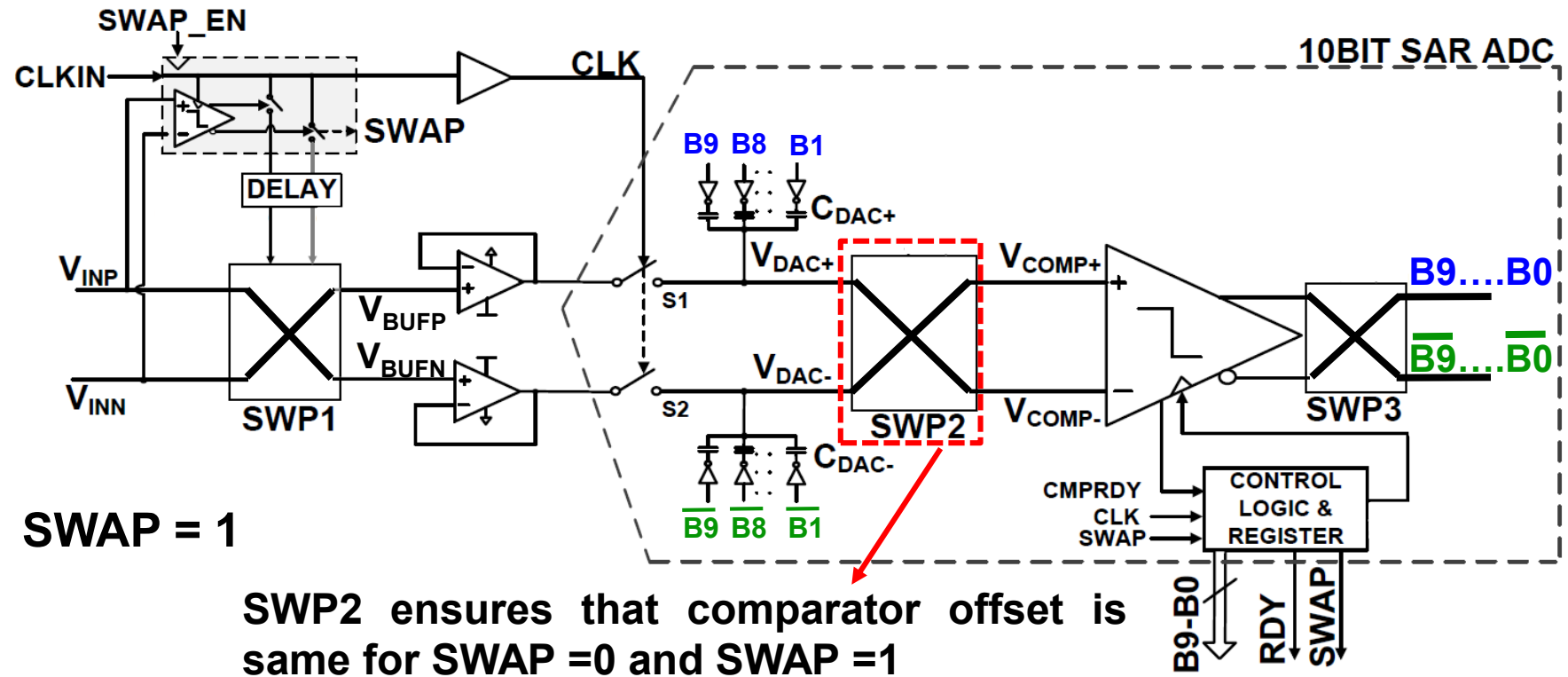
# Architecture - Buffers integrated with ADC



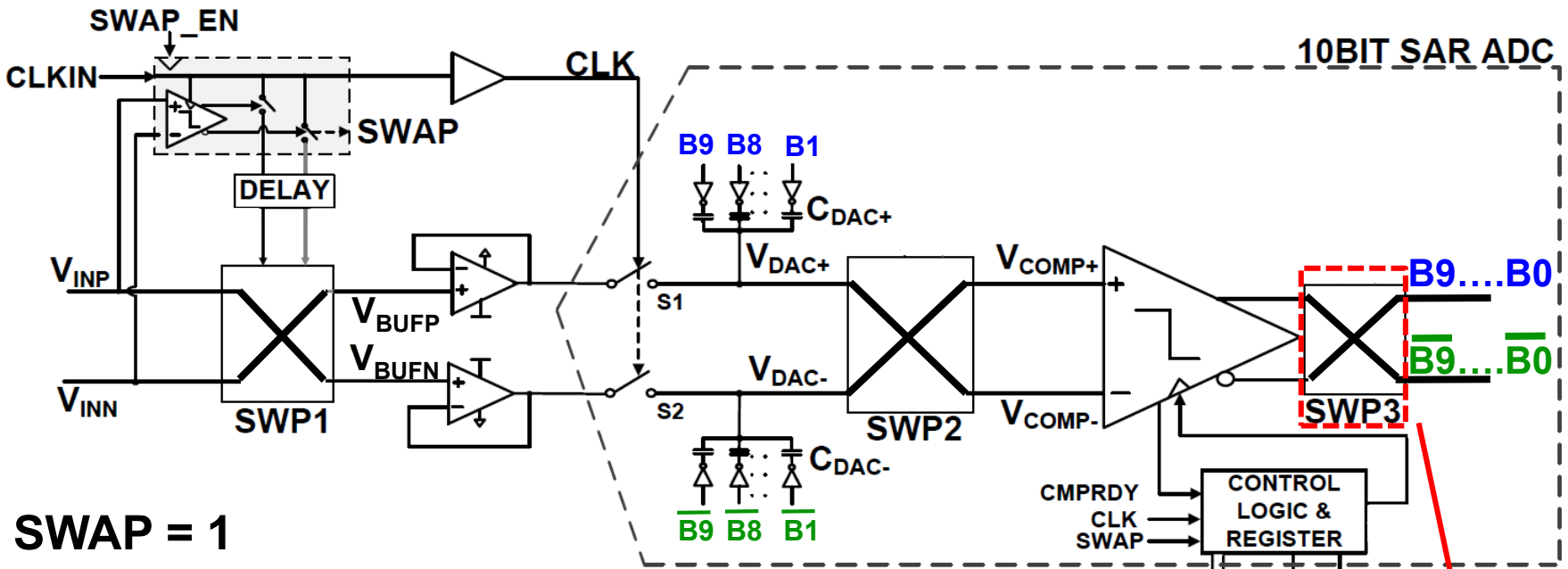
# Architecture - Buffers integrated with ADC




**SWAP = 1**

**SWP3 keeps SAR loop convergent**
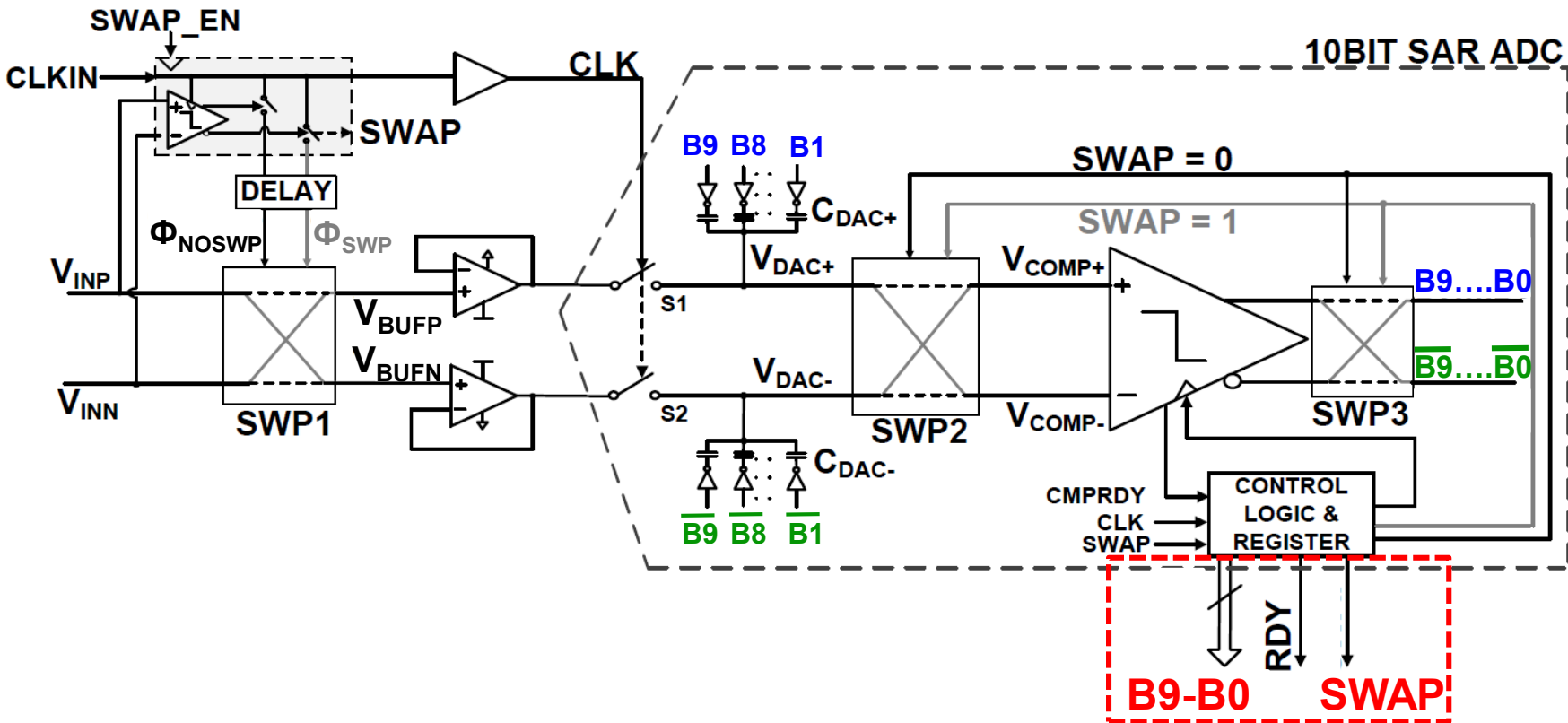
# Architecture - Buffers integrated with ADC


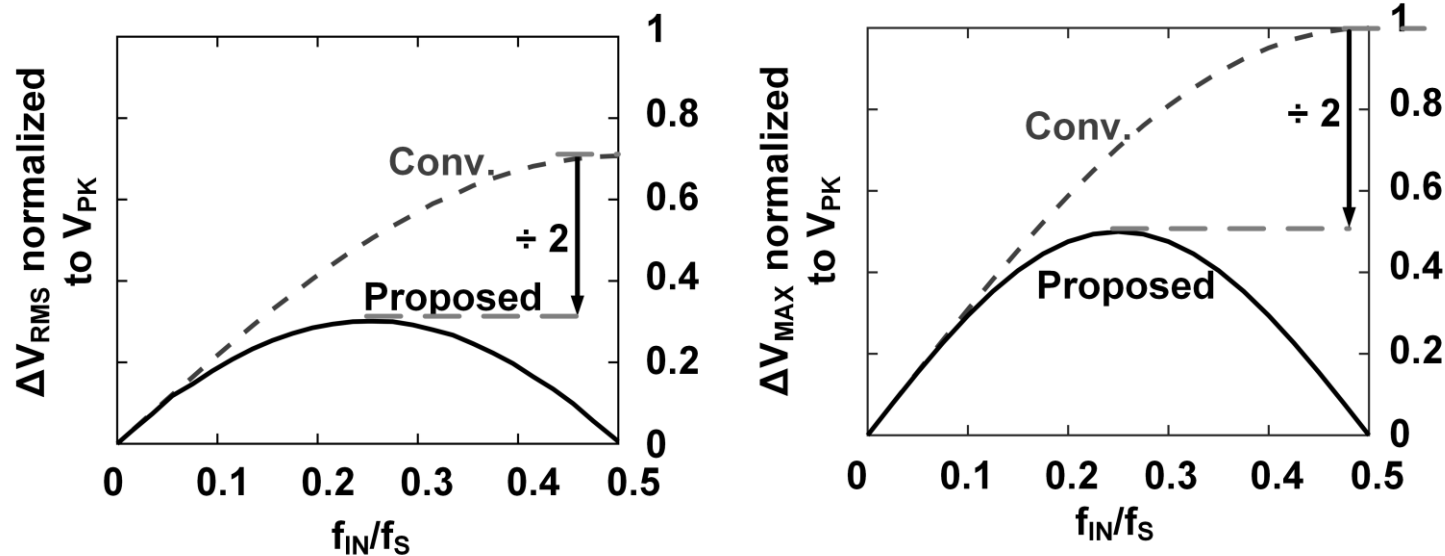
# Change in voltage ( $V_{\text{BUF}}$ and $V_{\text{CDAC}}$ )




- MATLAB simulated RMS and maximum change in voltage at the buffer input
  - **Reduced by 2x compared to conventional sampling**
  - **$E_{\text{IN}} = C_{\text{IN}} \cdot \Delta V_{\text{BUFP}} \cdot V_{\text{DD}}$  is also reduced by 2x**

# Overview


- Motivation
  - Input Buffer Requirement
- Reducing Input Drive Current
- **Low power single supply buffered SAR ADC (CICC 2019)**
  - Proposed Solution
  - Integration of Buffer with SAR ADC
  - **Offset Correction**
- Measurement Results
- Conclusion

# Architecture - Offset Correction

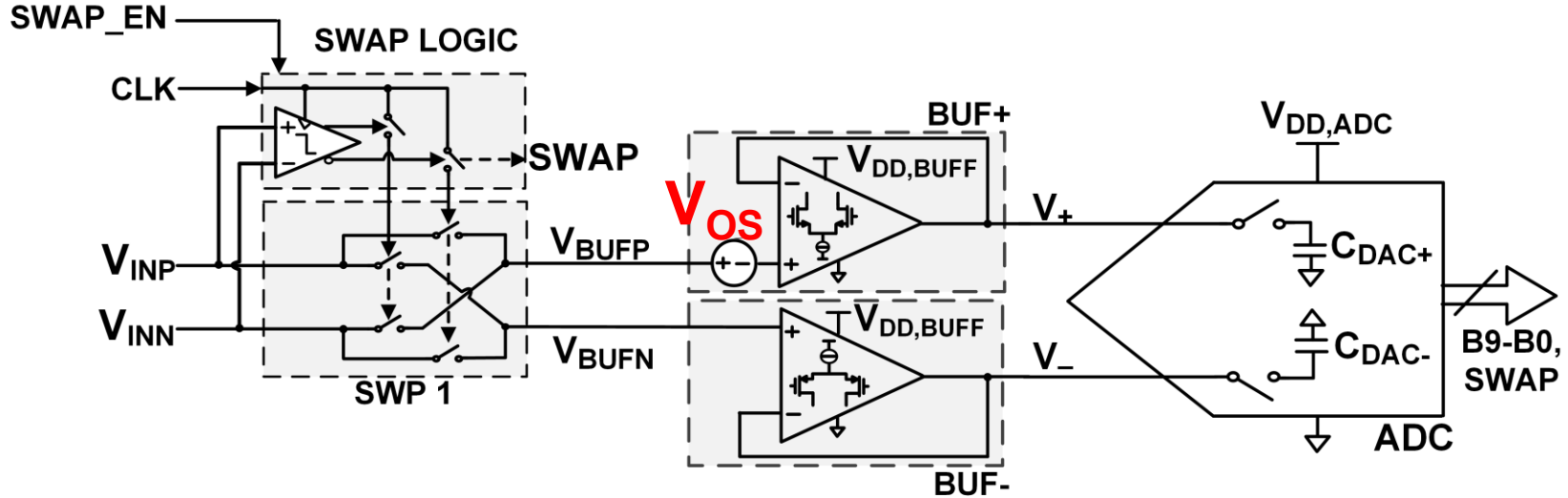

$V_{OS}$  : offset mismatch between BUF+ and BUF-


# Architecture - Offset Correction

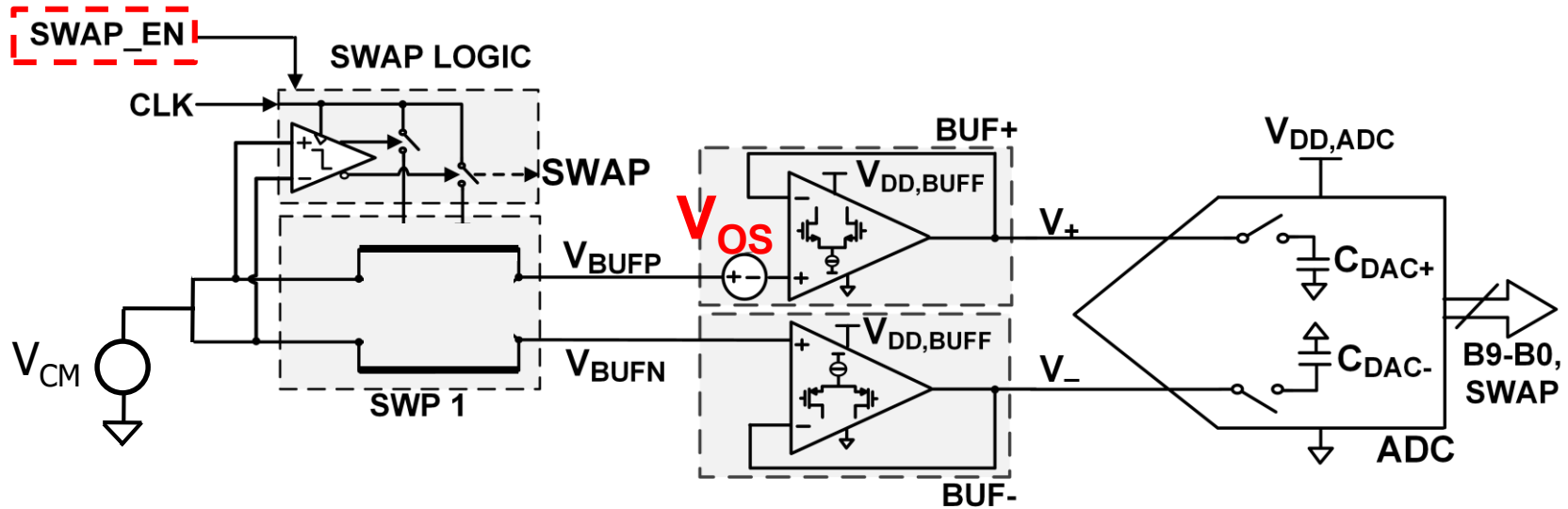

$B_{OUT,OS}$  : estimated by disabling SWAP and applying  
 $V_{INP} - V_{INN} = 0$ .



# Architecture - Offset Correction

 


$$B_{OUT,SWAP} = \overline{B_{OUT} - B_{OUT,OS}}$$
$$B_{OUT,NOSWAP} = B_{OUT} - B_{OUT,OS}$$

# Overview

- **Motivation**
  - Input Buffer Requirement
- **Reducing Input Drive Current**
- **Low power single supply buffered SAR ADC**
  - Proposed Solution
  - Integration of Buffer with SAR ADC
  - Offset Correction
- **Measurement Results**
- **Conclusion**


# Die micrograph (65nm CMOS)

 


Area : 0.075mm<sup>2</sup>  
(incl. decaps)

Power Consumption  
ADC : 9µW  
Buffers : 70µW each


# Measurement Results - FFT

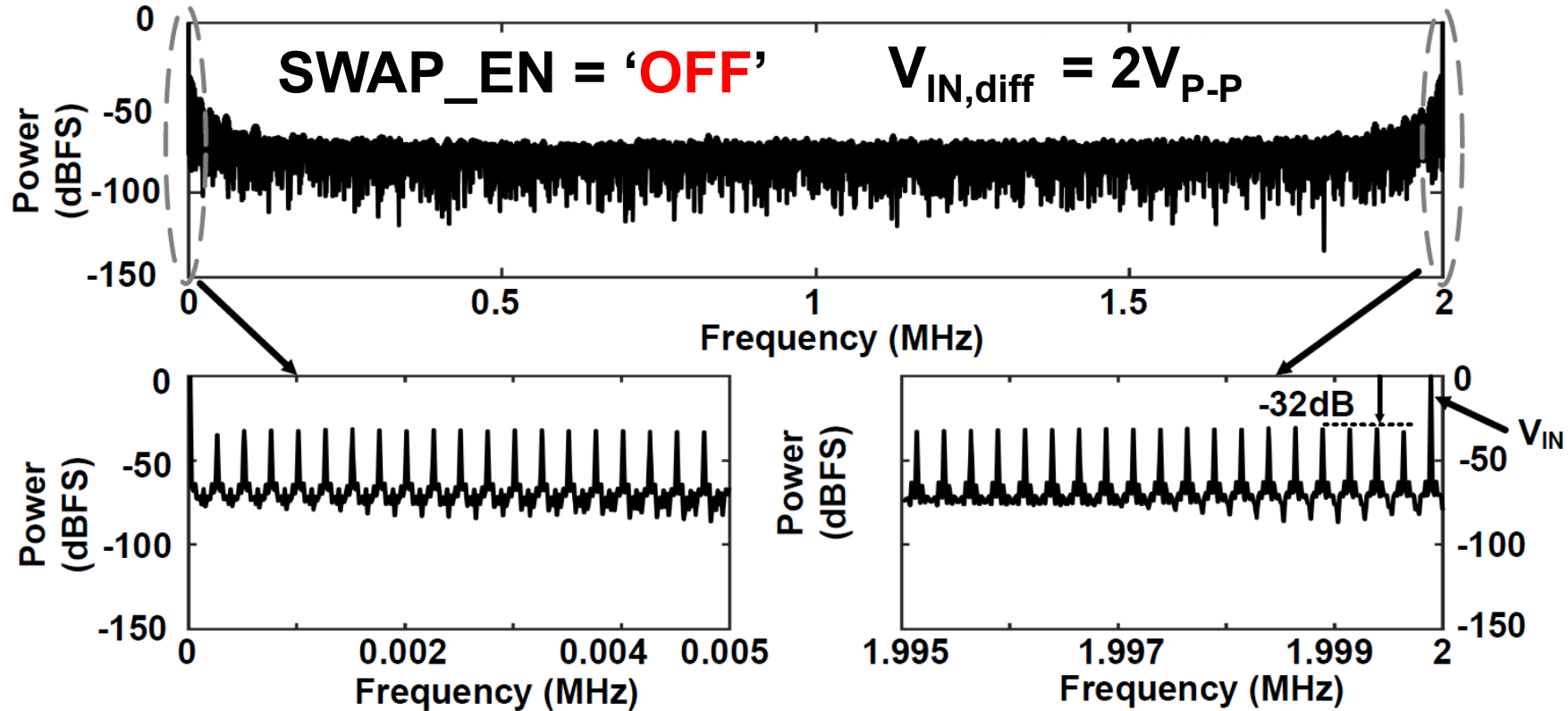

# Measurement Results - FFT

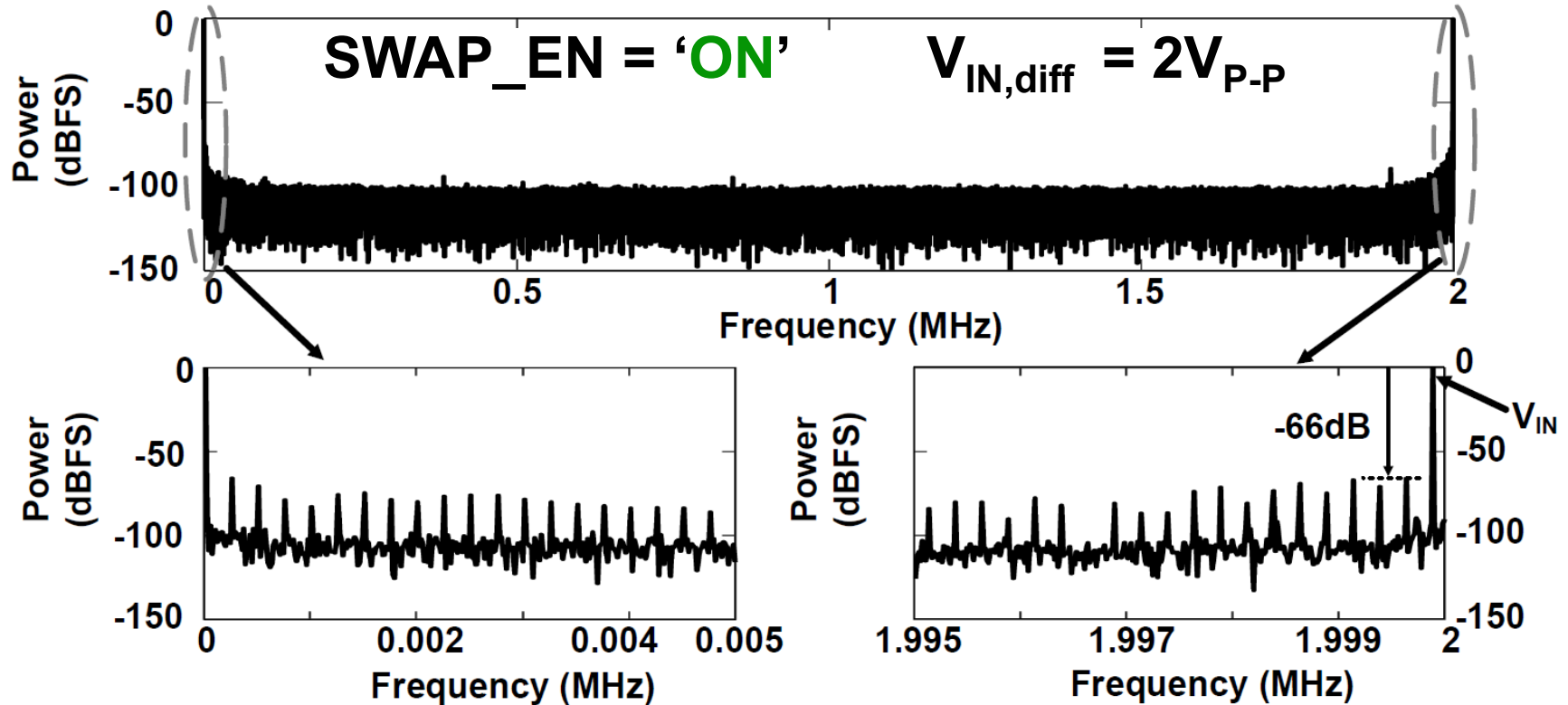


# Measurement Results - INL/DNL

 


- $f_s = 4\text{MS/s}$
- **INL = 1.2LSB**
- **DNL = 0.5LSB**

# Measurement Results - INL/DNL

 

- **Maximum jump is at mid-code due to non-segmented DAC array**

# Measurement Results – SFDR/SNDR

 

- $f_s = 4\text{MS/s}$
- SFDR > 64dB over Nyquist range
- SNDR > 54dB over Nyquist range



# Table of Comparison

Architecture		This Work	Krämer ISSCC 2015	Tseng JSSC 2016
Technology (nm)		65	40	28
Supply [V]	ADC	1.2	1.2	1.1
	Buffer		2.5	1.2
Diff. Input Signal ( $V_{PK-PK}$ )		2	1.8	1.2
Maximum Sampling Rate (MS/s)		4	35	100
Power Consumption (ADC+Buffer) in mW		0.149	54.5	3.1
ENOB [bits]		8.7	12.1	7.2
FoM <sub>w</sub> (fJ/conversion) = $(P_{ADC} + P_{Buffer}) / 2^{ENOB} \cdot f_s$		87	355	200
Area (in mm <sup>2</sup> )		0.075 (incl. decap)	0.24 (incl. decap)	0.024 (Core only)

# Overview

- **Motivation**
  - Input Buffer Requirement
  - Prior Art
- **Architecture**
  - Proposed Solution
  - Integration of Buffer with SAR ADC
  - Offset Correction
- **Measurement Results**
- **Conclusion**

# Conclusion

- **Buffers and ADC operate at single supply voltage (1.2V) while processing near rail-to-rail inputs.**
- **Swapping the inputs allow each of the input buffer to handle one-half the full-scale range.**
- **State-of-the-art Walden FoM (ADC+Buffer) of 87fJ/conv-step.**